

SCHOOL OF ENGINEERING, ELECTRICAL AND ELECTRONIC ENGINEERING

NETWORKS 4_

Week D_



Ronald van Buuren
May 2023

NET4 PROGRAM BY WEEK


1. 1st order RC networks – discharging – DC source
2. 1st order RC networks – charging –DC source
3. RL networks – Steady-state DC
4. RL networks – Switched DC source
5. RC & RL networks – complementary solution
6. <spare week>
7. Sample Exam

CAPACITOR & INDUCTOR RELATIONS

	Capacitor	Inductor
Voltage	$v = \frac{1}{C} \int i(t) dt$	$v = L \frac{di}{dt}$
Current	$i = C \frac{dv}{dt}$	$i = \frac{1}{L} \int v(t) dt$
Power	$P(t) = v(t) \cdot i(t)$	
Energy	$W(t) = \frac{1}{2} C v^2(t)$	$W(t) = \frac{1}{2} L i^2(t)$
Energy stored in:	Electric field	Magnetic field


WEEK C: DC STEADY STATE

At $t = 0$ we close the switch

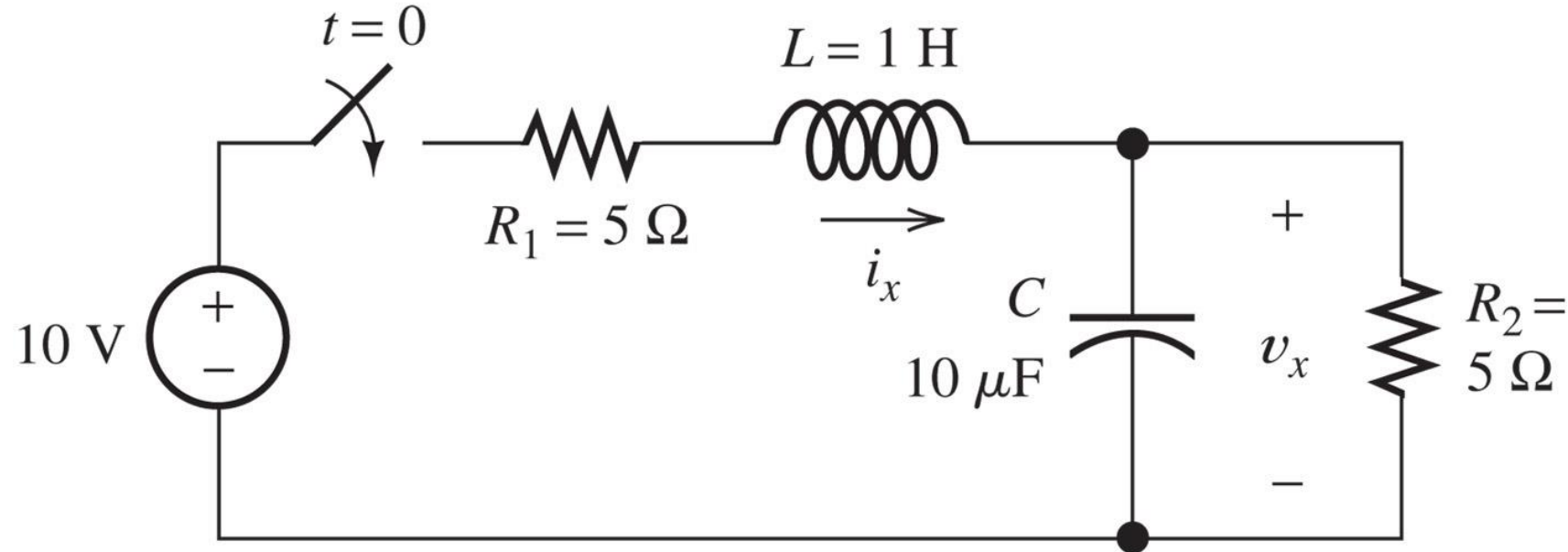

WEEK C: DC STEADY STATE

Equivalent circuit at $t = \infty$

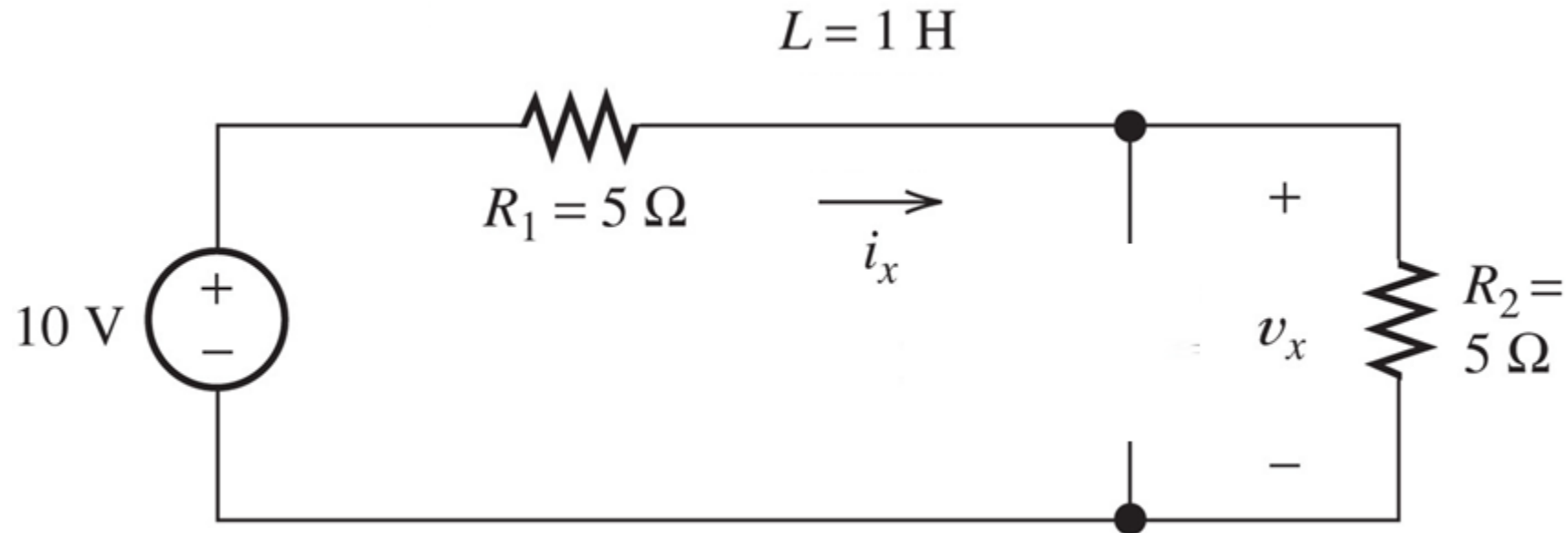


$$i_x = V / (R_1 + R_2) = 1\ \text{A}$$

$$v_x = R_2 / (R_1 + R_2) \times V = 5\ \text{V (voltage division)}$$

RL CIRCUITS


Find expressions for $i(t)$ and $v(t)$ for $t > 0$

- probably a differential equation?

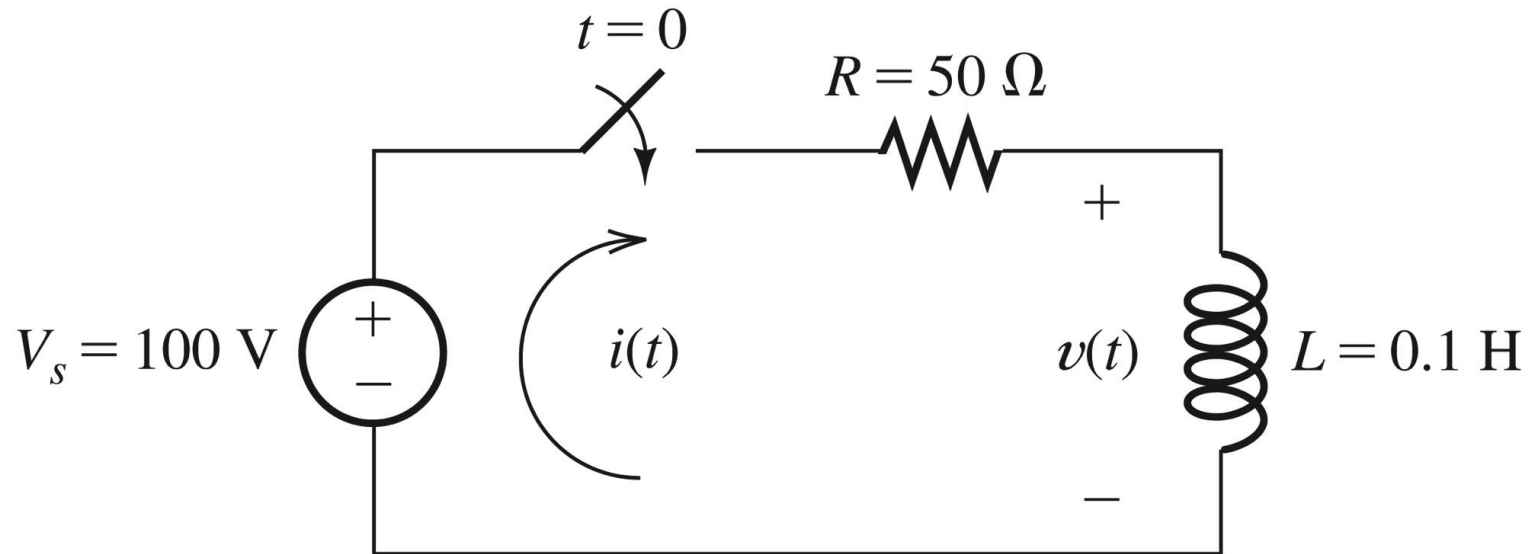

Copyright ©2018 Pearson Education, All Rights Reserved.

RL CIRCUITS - USING KVL

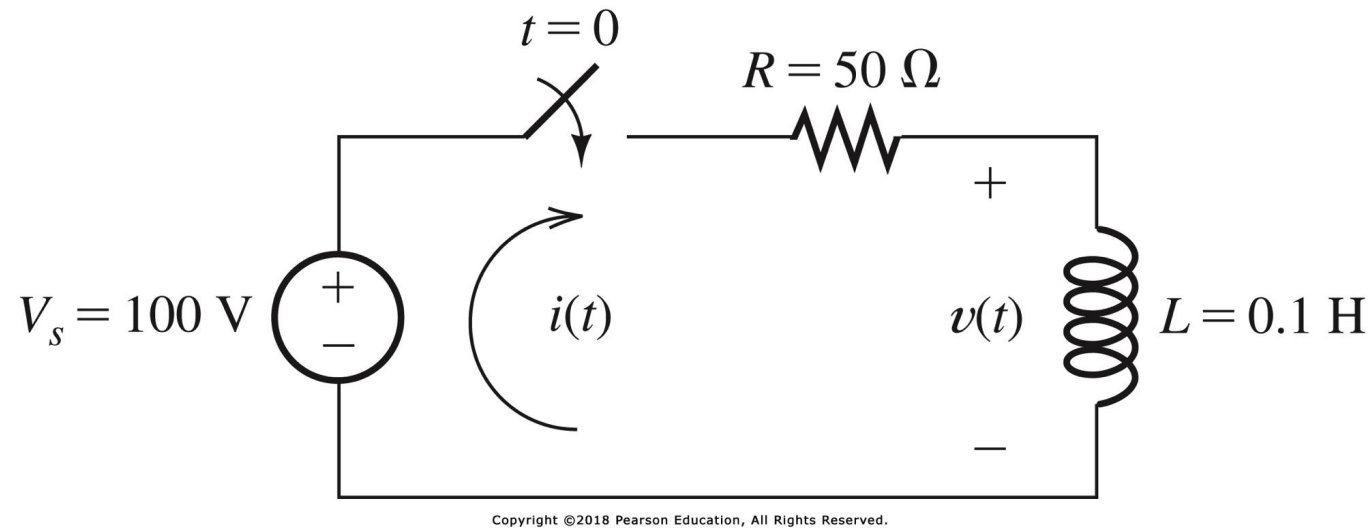

1. KVL: Write individual voltages *with polarities*

a) $+V_s$

b) $v_R = -i(t) \cdot R$

c) $v_L = -L di/dt$

2. Write KVL:

$$V_s - i(t) \cdot R - L di/dt = 0$$

3. Re-arrange:


$$i(t) + \frac{L}{R} \frac{di(t)}{dt} = \frac{V_s}{R}$$

Inductor

$$v = L \frac{di}{dt}$$

Haven't we seen this before?

RL CIRCUITS - USING KVL

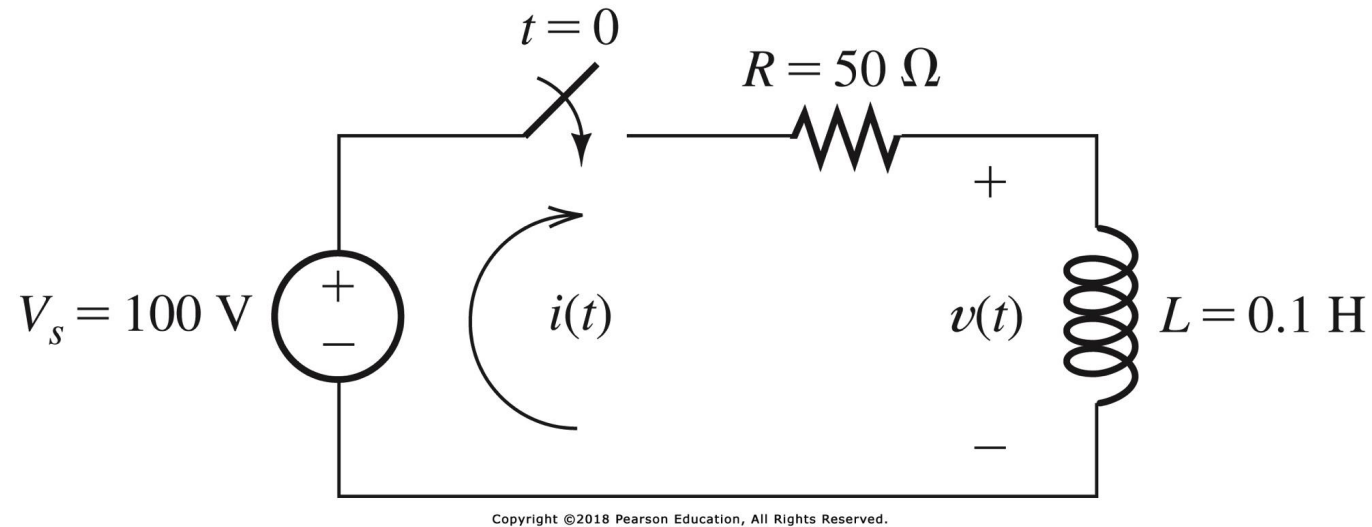

$$i(t) + \frac{L}{R} \frac{di(t)}{dt} = \frac{V_s}{R}$$

Inductor


$$v = L \frac{di}{dt}$$

Remember week B, charging a capacitor (and KCL):

$$C \frac{dv_C(t)}{dt} + \frac{v_C(t) - V_s}{R} = 0$$

Educated guess $i = K_1 + K_2 e^{st}$

RL CIRCUITS - USING KVL

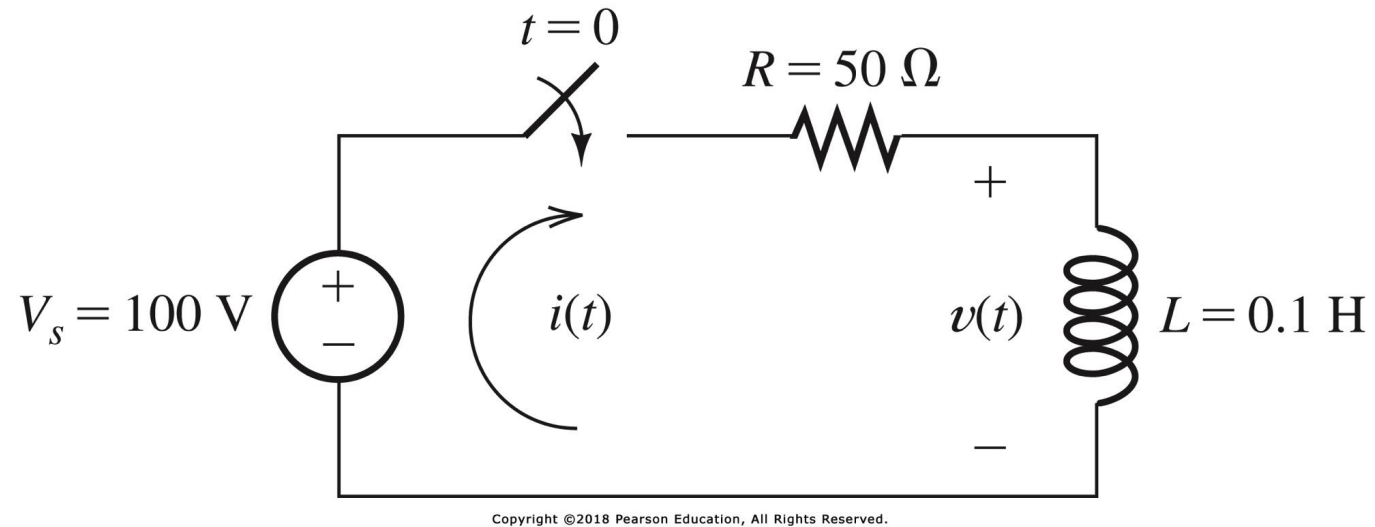


$$i(t) + \frac{L}{R} \frac{di(t)}{dt} = \frac{V_s}{R}$$

insert $i(t) = K_1 + K_2 e^{st}$:


$$K_1 + K_2 e^{st} + \frac{L}{R} s K_2 e^{st} = \frac{V_s}{R}$$

RL CIRCUITS - USING KVL

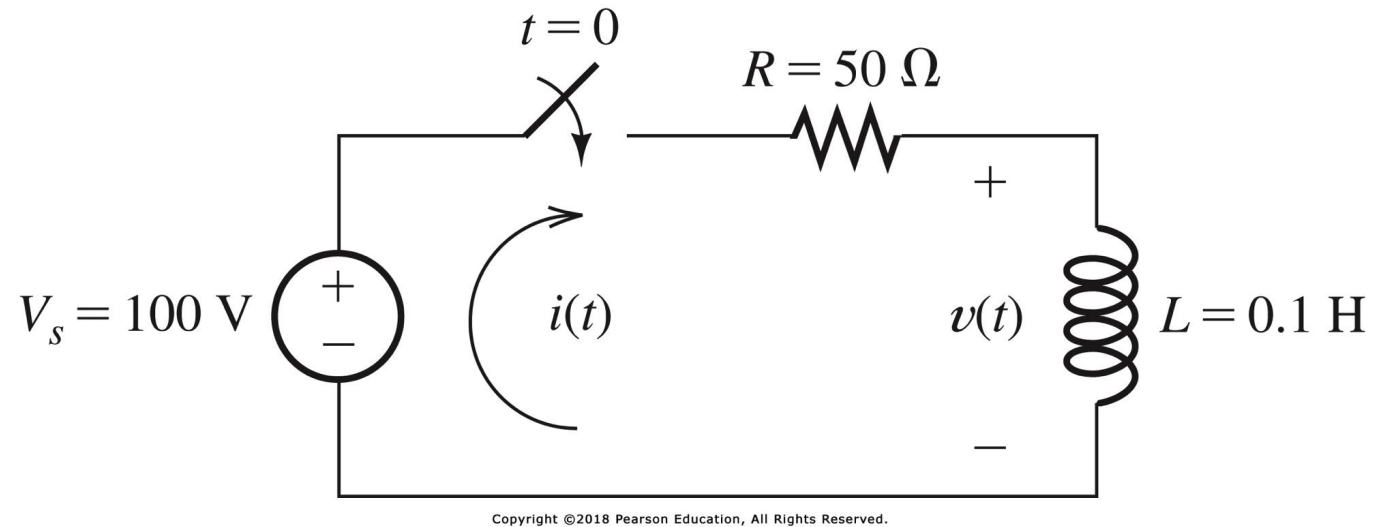

$$K_1 + K_2 e^{st} + \frac{L}{R} s K_2 e^{st} = \frac{V_s}{R}$$

RL CIRCUITS - USING KVL

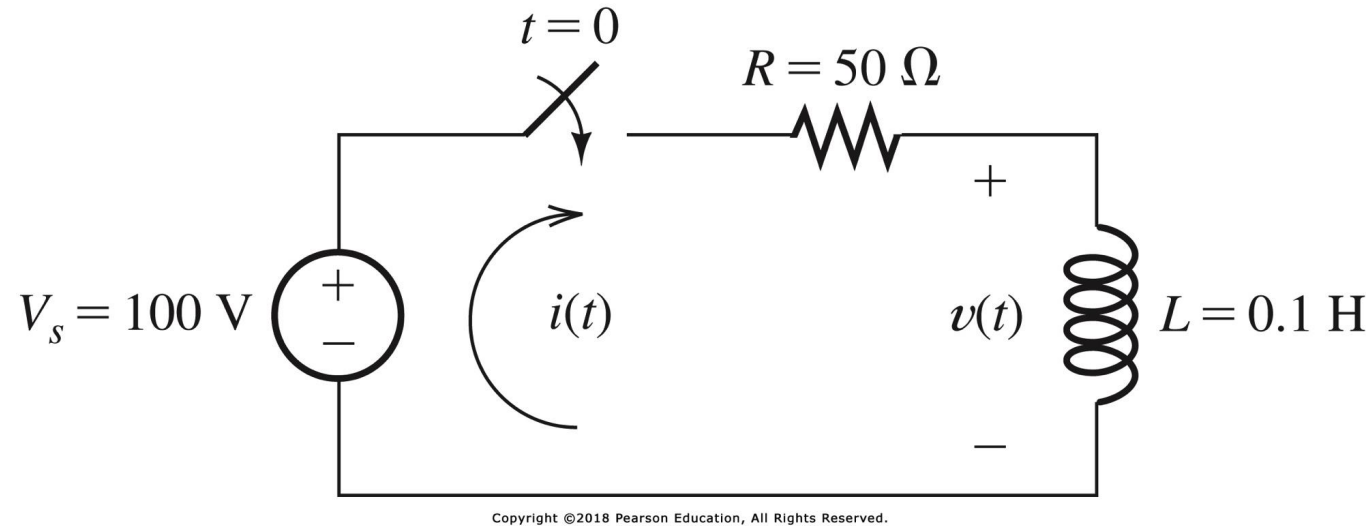

$$K_1 + K_2 e^{st} + \frac{L}{R} s K_2 e^{st} = \frac{V_S}{R}$$

$$K_1 = \frac{V_S}{R} = 2 \text{ A}$$

$$s = -\frac{R}{L} = -500 \text{ s}^{-1}$$

$$\tau = \frac{L}{R}$$

$K_2?$

Aha, *initial condition around $t=0$*


- i. $i(t=0^-) = 0$
- ii. $i(t=0^+) = 0$ (i must be continuous)
- iii. So, $K_2 = -K_1 = -2 \text{ A}$

$$i(t) = K_1 + K_2 e^{st}$$


$$i(t) = 2 - 2e^{-500t} \text{ A}$$

$$i(t) = 2 - 2e^{-500t} \text{ A}$$

	A	B	C	D
1	t [ms]	i(t)		
2	0,1	0,097541		
3	0,2	0,190325		
4	0,3	0,278584		
5	0,4	0,362538		
6	0,5	0,442398		
7	0,6	0,518364		
8	0,7	0,590624		
9	0,8	0,65936		
10	0,9	0,724744		
11	1	0,786939		
12	1,1	0,8461		
13	1,2	0,902377		
14	1,3	0,955908		
15	1,4	1,006829		
16	1,5	1,055267		
17	1,6	1,101342		

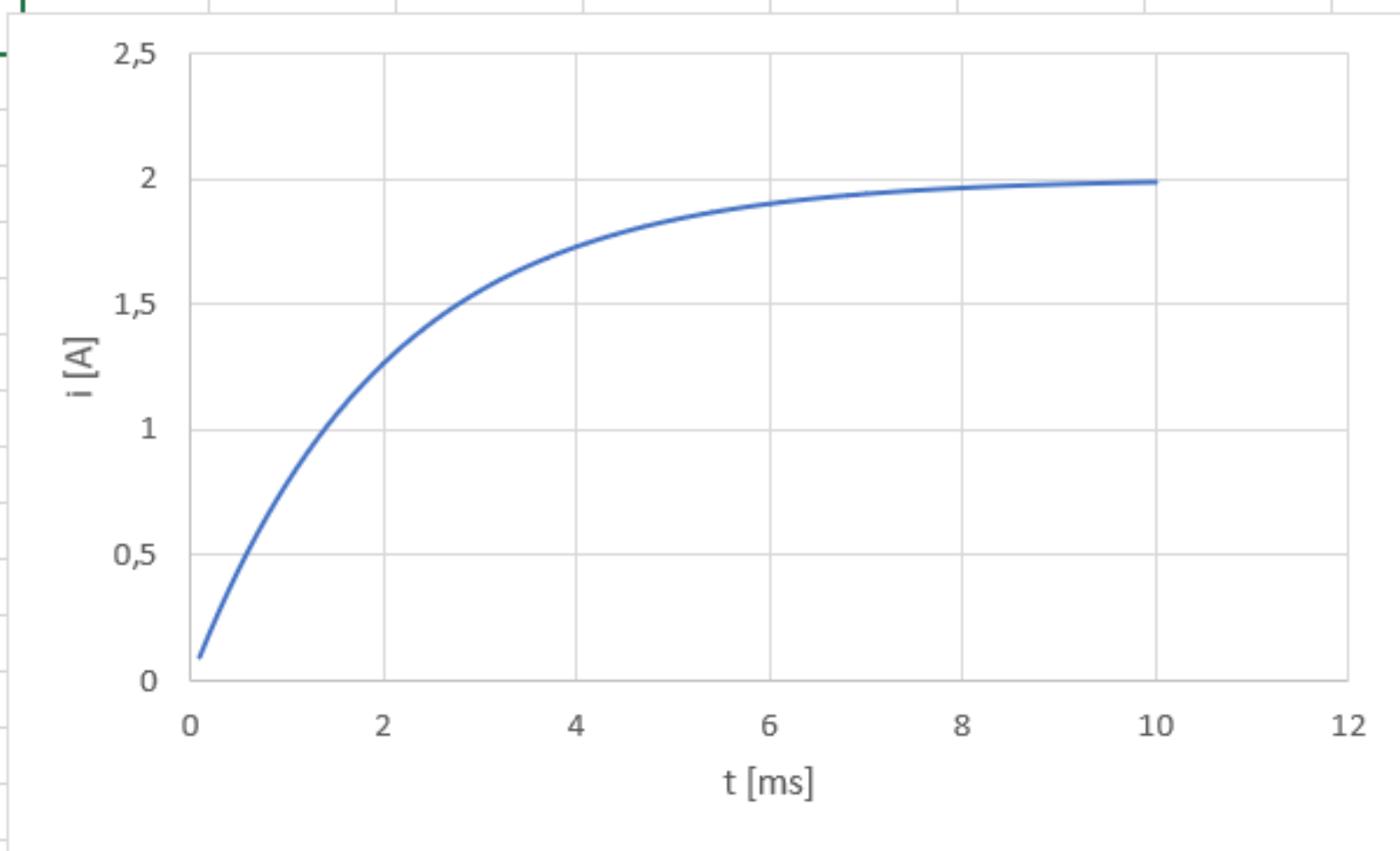

RL CIRCUITS - USING KVL

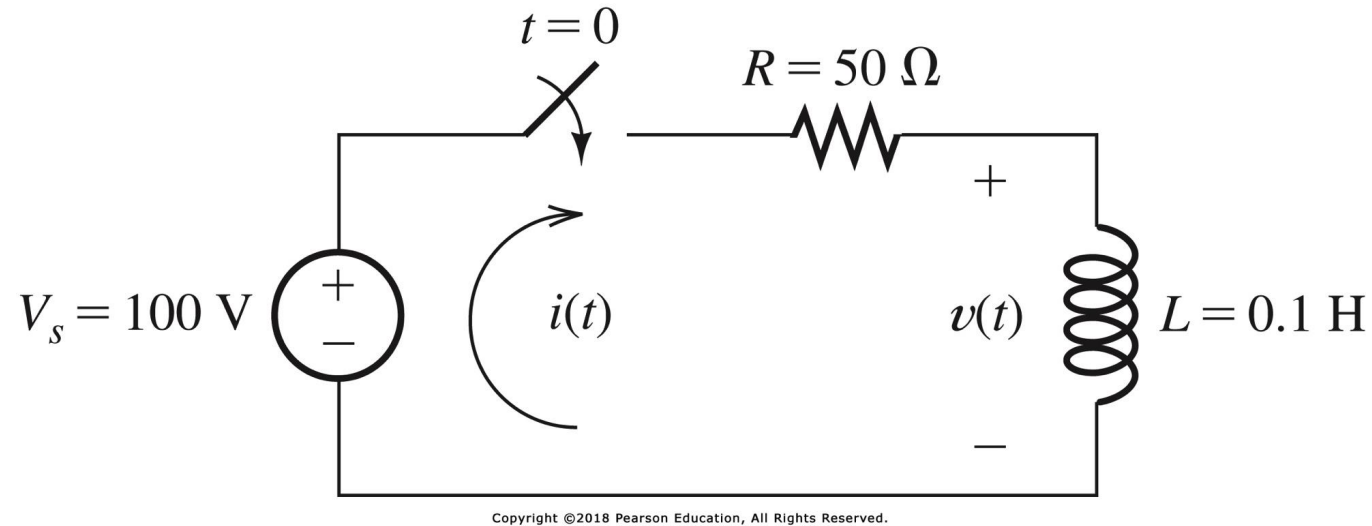

Final step: find $v(t)$

$$i(t) = 2 - 2e^{-500t} \text{ A}$$

so (how's your Math?)


$$0.1 \cdot d(2 - 2e^{-500t})/dt$$

$$v(t) = 100e^{-500t} \text{ V}$$

Inductor

$$v = L \frac{di}{dt}$$

	A	B	C	D	E	F	G	H	I	J	K	L
1	t [ms]	i(t)	v(t)									
2	0,1	0,097541	95,12294245									
3	0,2	0,190325	90,4837418									
4	0,3	0,278584	86,07079764									
5	0,4	0,362538	81,87307531									
6	0,5	0,442398	77,88007831									
7	0,6	0,518364	74,08182207									
8	0,7	0,590624	70,46880897									
9	0,8	0,65936	67,0320046									
10	0,9	0,724744	63,76281516									
11	1	0,786939	60,65306597									
12	1,1	0,8461	57,69498104									
13	1,2	0,902377	54,88116361									
14	1,3	0,955908	52,20457768									
15	1,4	1,006829	49,65853038									
16	1,5	1,055267	47,23665527									
17	1,6	1,101342	44,93289641									
18	1,7	1,14517	42,74149319									
19	1,8	1,186861	40,65606507									

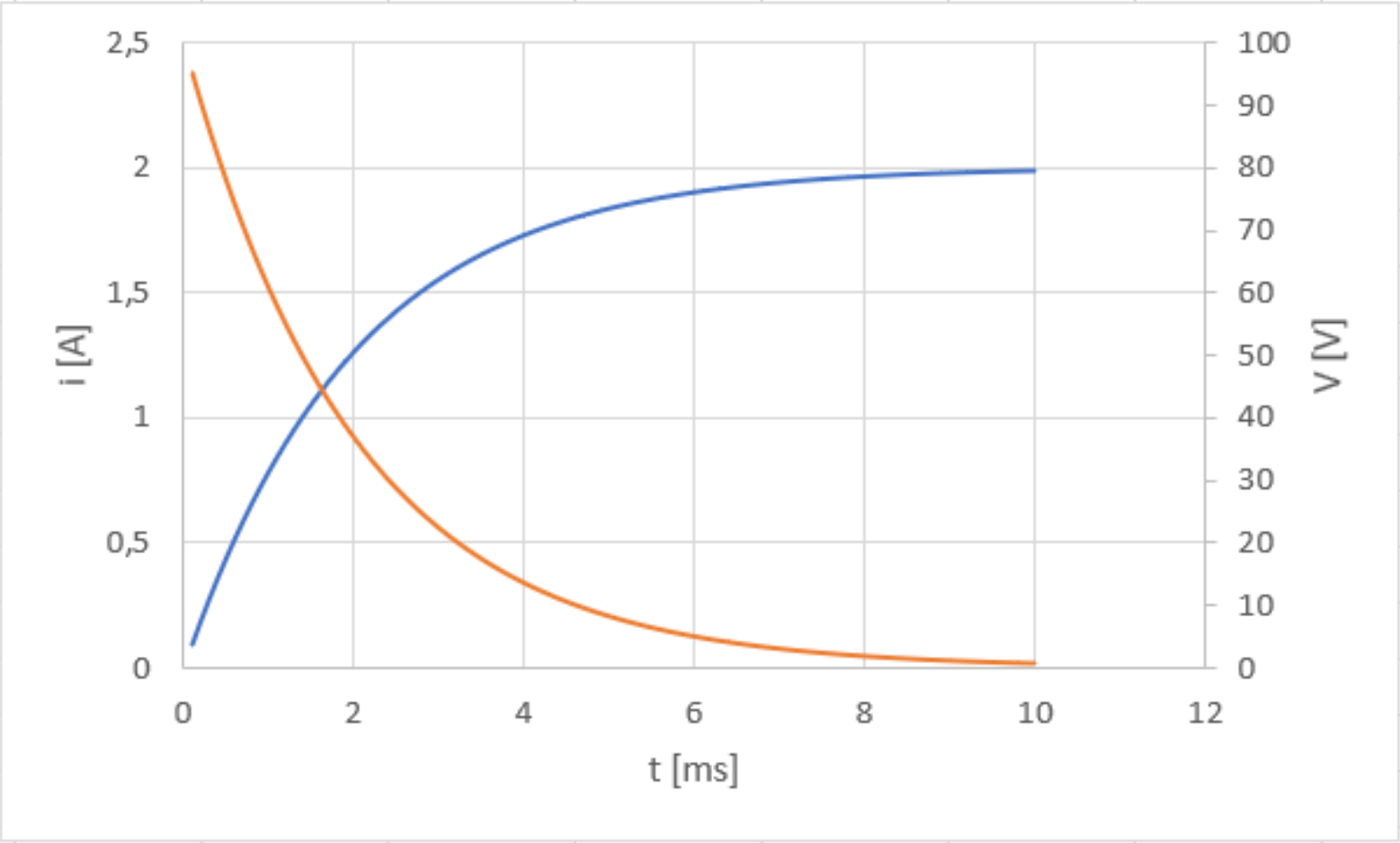


RECIPE FOR SIMPLE CIRCUITS (RC & RL)

1. Use one of Kirchhoff's laws to get a circuit equation
2. If the equation has integrals, differentiate all terms to get a pure differential equation
3. Try a solution of the type $K_1 + K_2 e^{st}$
 1. Enter it into the equation
 2. Solve for K_1 & s
 3. Use starting conditions ($t=0^-$, $t=0^+$) to get K_2
4. Write the now fully known equation
 1. i.e. using R , L , C , τ

RL CIRCUITS – NOW VIA KCL


Find expressions for $i(t)$ and $v(t)$ for $t > 0$

- surely another differential equation

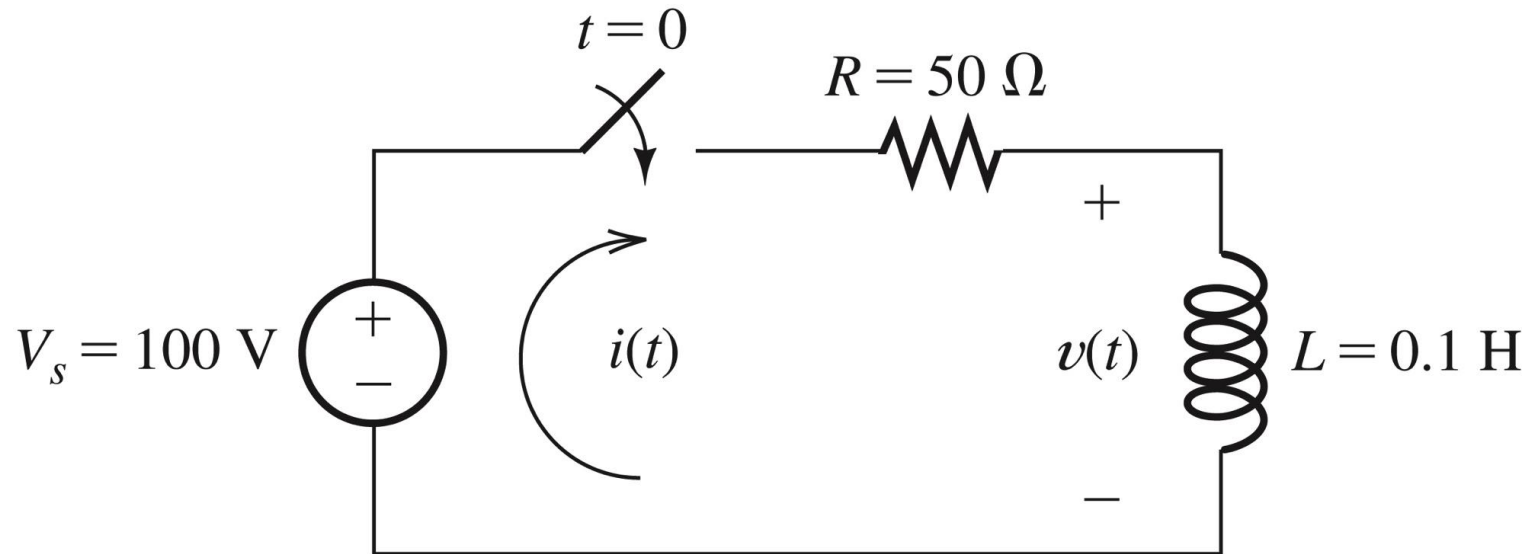

Copyright ©2018 Pearson Education, All Rights Reserved.

RL CIRCUITS – NOW VIA KCL

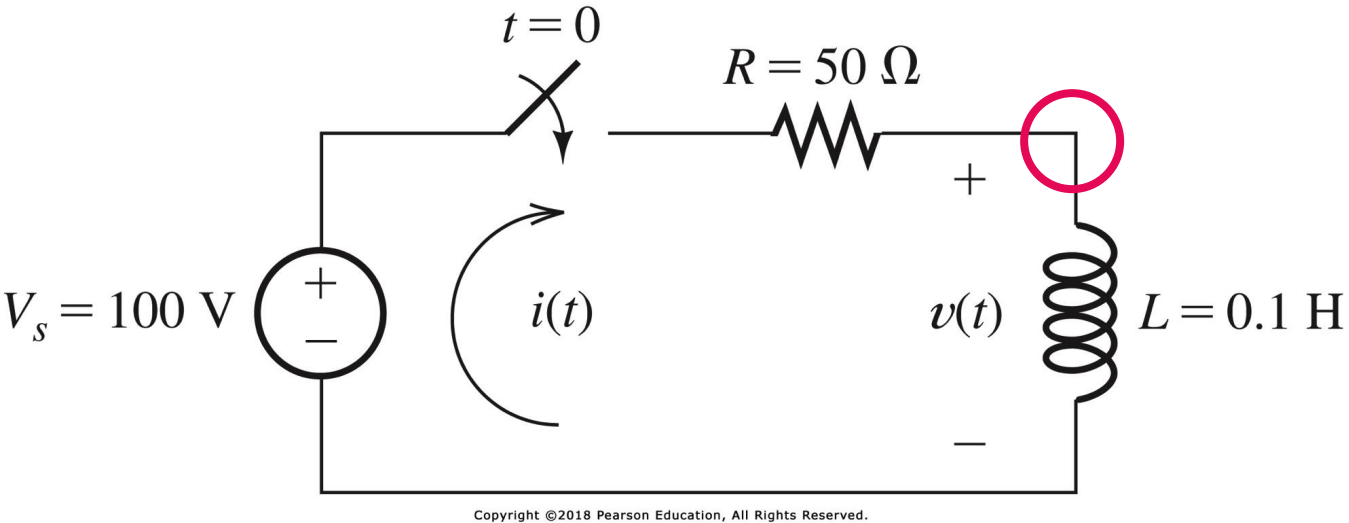

1. Write individual currents *with polarities*

a) $i_R = (V_s - v(t)) / R$

b) $i_L = -\frac{1}{L} \int v(t) dt$

$$i = \frac{1}{L} \int v(t) dt$$

2. Apply KCL: **sum = 0 @ node**

$$[V_s - v(t)]/R - \frac{1}{L} \int v(t) dt = 0$$


3. Differentiate to remove integral:

$$0 - \frac{1}{R} \frac{dv(t)}{dt} - \frac{1}{L} v(t) = 0$$

4. Rearrange:

$$v(t) + \frac{L}{R} \frac{dv(t)}{dt} = 0$$

RL CIRCUITS – NOW VIA KCL

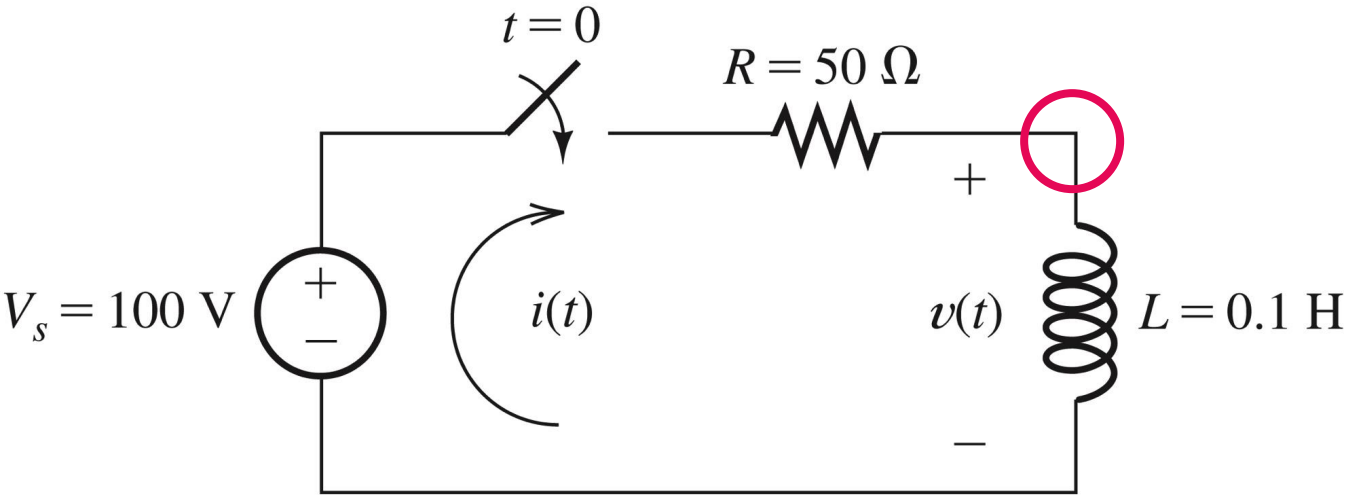

Copyright ©2018 Pearson Education, All Rights Reserved.

$$v(t) = 100e^{-500t} \text{ V}$$

$$v(t) + \frac{L}{R} \frac{dv(t)}{dt} = 0$$

$$\text{Try } v = K_1 + K_2 e^{st}$$

$$K_1 + K_2 e^{st} + \frac{L}{R} s K_2 e^{st} = 0$$


$$K_1 = 0$$

$$s = -\frac{R}{L}$$

$$\text{Initial: } v(0+) = V_s = 100 \text{ V}$$

$$K_2 = 100 \text{ V}$$

RL CIRCUITS – NOW VIA KCL

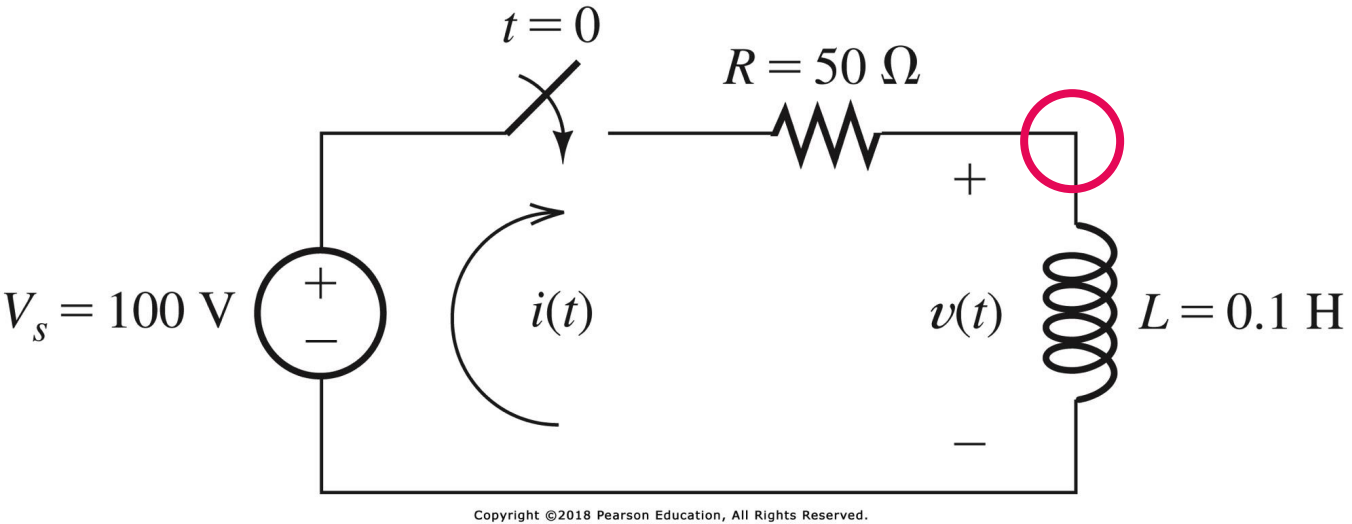

Final step: find $i(t)$

$i(t)$ is the same everywhere, so choose R to get it using Ohm's law


$$\begin{aligned} i(t) &= (V_s - v(t)) / R \\ &= (100 - 100e^{-500t}) / 50 \end{aligned}$$

$$i(t) = 2 - 2e^{-500t} \text{ A}$$

$$v(t) = 100e^{-500t} \text{ V}$$

RL CIRCUITS – VIA DC STEADY STATE


will follow later

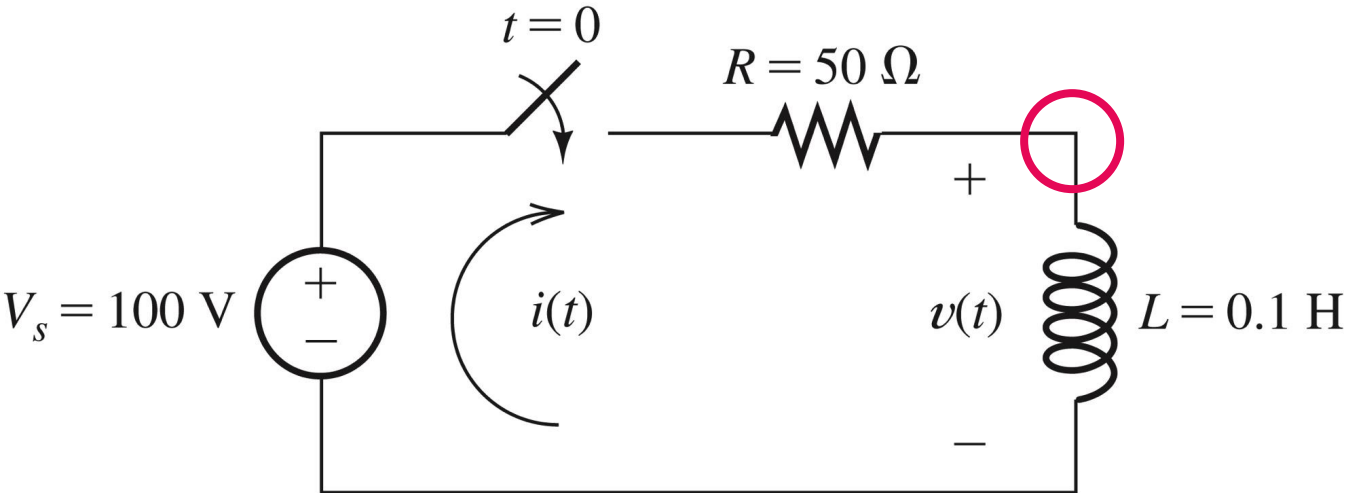

Copyright ©2018 Pearson Education, All Rights Reserved.

EXERCISE

Find $i(t)$ and $v(t)$ for $t > 0$

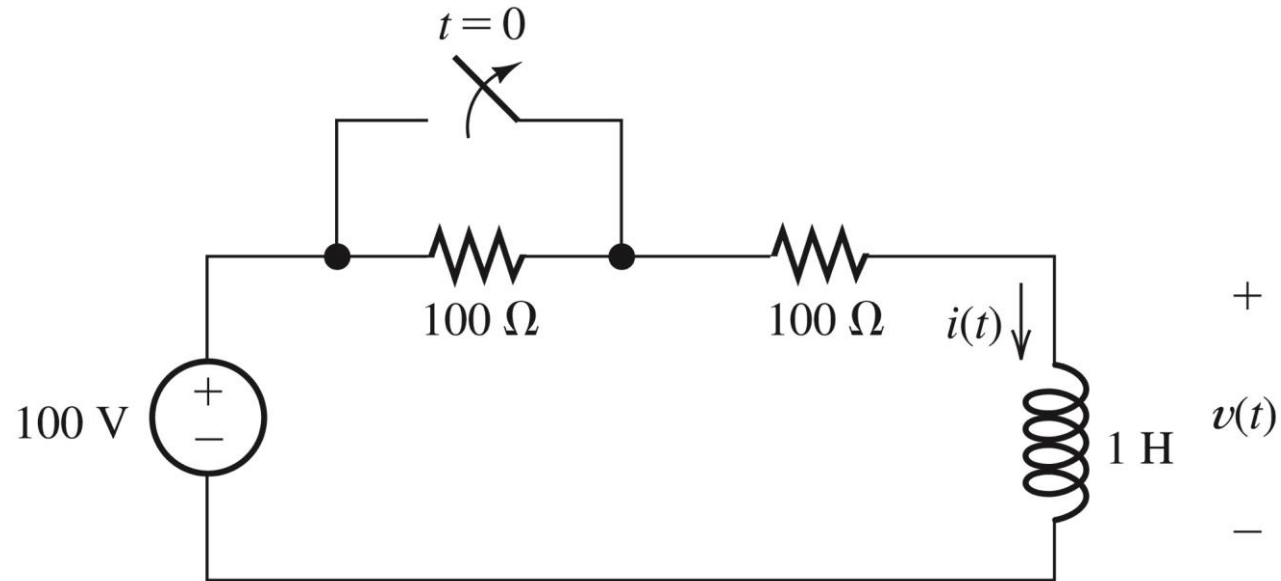

Copyright ©2018 Pearson Education, All Rights Reserved.

PROBLEMS FOR THE EXERCISES SESSION

- P4.31
- P4.33
- P4.34
- P4.37
- P4.39
- P4.42