

SCHOOL OF ENGINEERING, ELECTRICAL AND ELECTRONIC ENGINEERING

NETWORKS 4_

Week C_



Ronald van Buuren
April 2023


NET4 PROGRAM BY WEEK

1. 1st order RC networks – discharging – DC source
2. 1st order RC networks – charging –DC source
3. RL networks – Steady-state DC
4. RL networks – Switched DC source
5. RC & RL networks – complementary solution
6. <spare week>
7. Sample Exam

CAPACITOR & INDUCTOR RELATIONS


	Capacitor	Inductor
Voltage	$v = \frac{1}{C} \int i(t) dt$	$v = L \frac{di}{dt}$
Current	$i = C \frac{dv}{dt}$	$i = \frac{1}{L} \int v(t) dt$
Power	$P(t) = v(t) \cdot i(t)$	
Energy	$W(t) = \frac{1}{2} C v^2(t)$	$W(t) = \frac{1}{2} L i^2(t)$
Energy stored in:	Electric field	Magnetic field

WEEK B: CHARGING A CAPACITOR

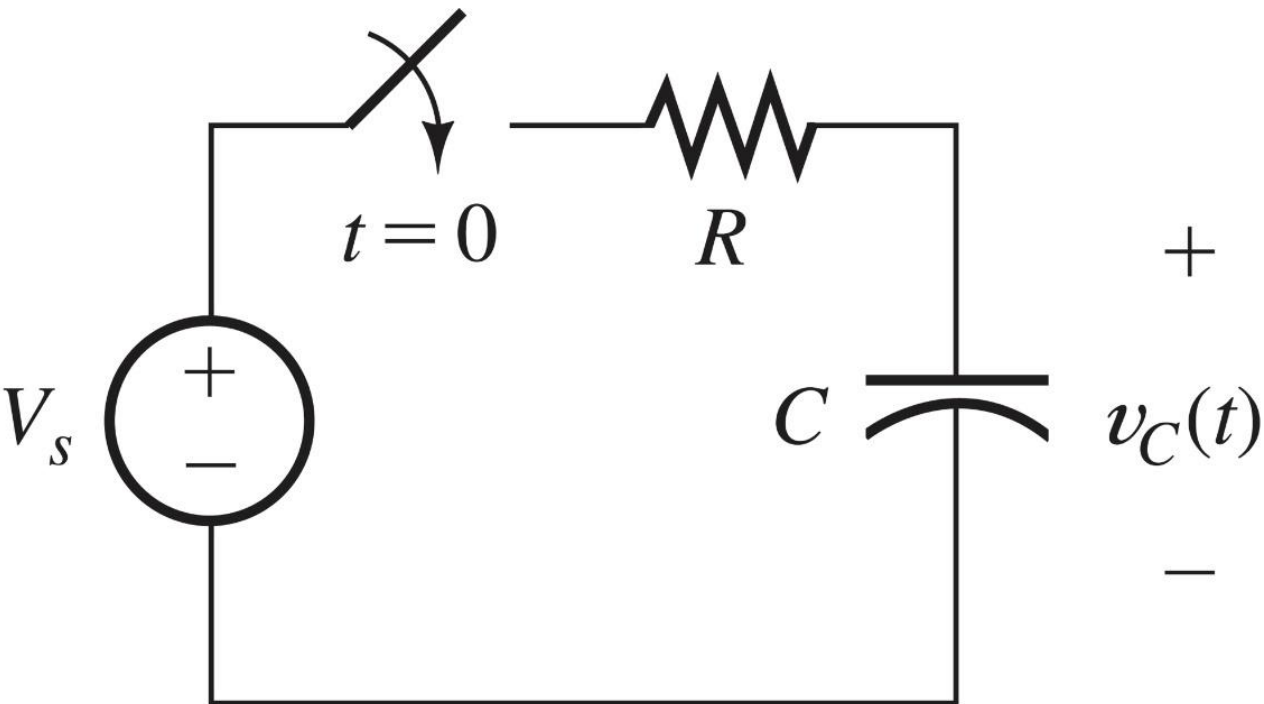

Copyright ©2018 Pearson Education, All Rights Reserved.
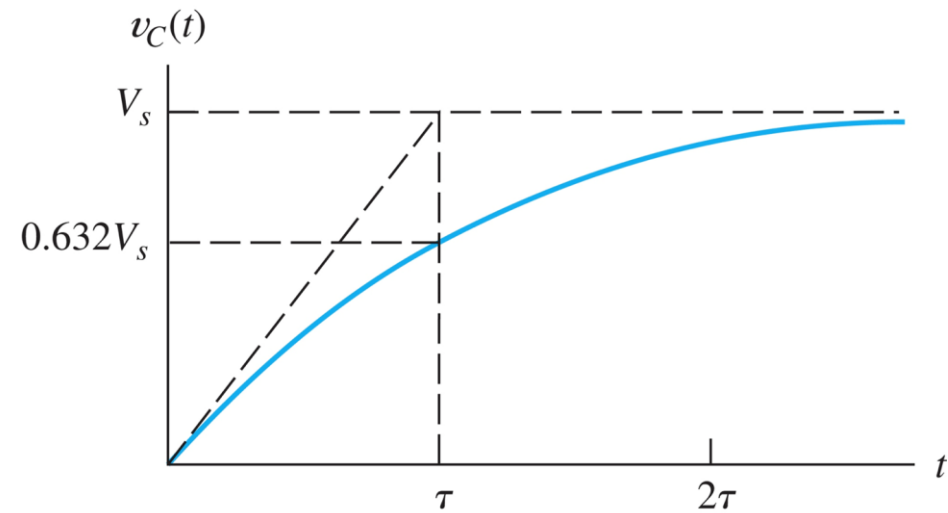
$$C \frac{dv_C(t)}{dt} + \frac{v_C(t) - V_s}{R} = 0$$



Copyright ©2018 Pearson Education, All Rights Reserved.

$$v_C(t) = V_s - V_s e^{-t/\tau}$$


$$\tau = RC$$

STEADY STATE

- Stable (steady) situation
- (at $t = \infty$)
- DC Steady State: circuit stabilises to fixed (DC) values
 - Inductor: consider to be a short circuit
 - Capacitor: consider to be open (i.e. no connection)


EXAMPLE: DC STEADY STATE

At $t = 0$ we close the switch

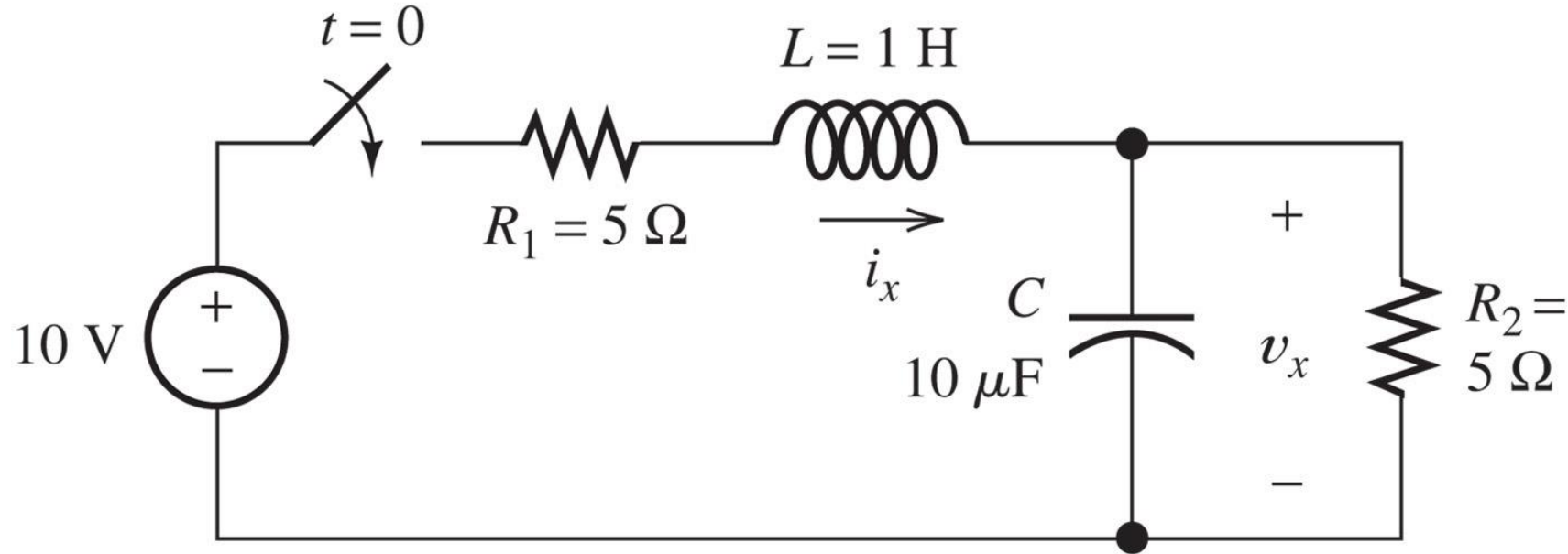

EXAMPLE SOLVED:

Equivalent circuit at $t = \infty$

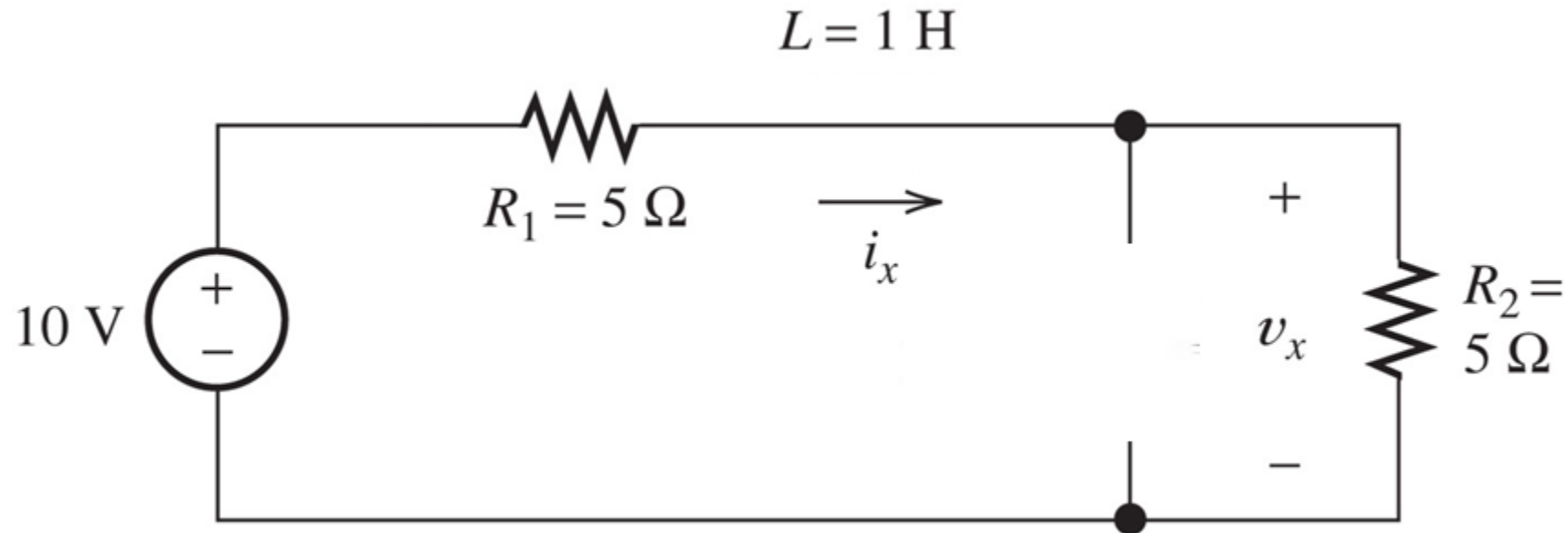


$$i_x = V / (R_1 + R_2) = 1 \text{ A}$$

$$v_x = R_2 / (R_1 + R_2) \times V = 5 \text{ V (voltage division)}$$

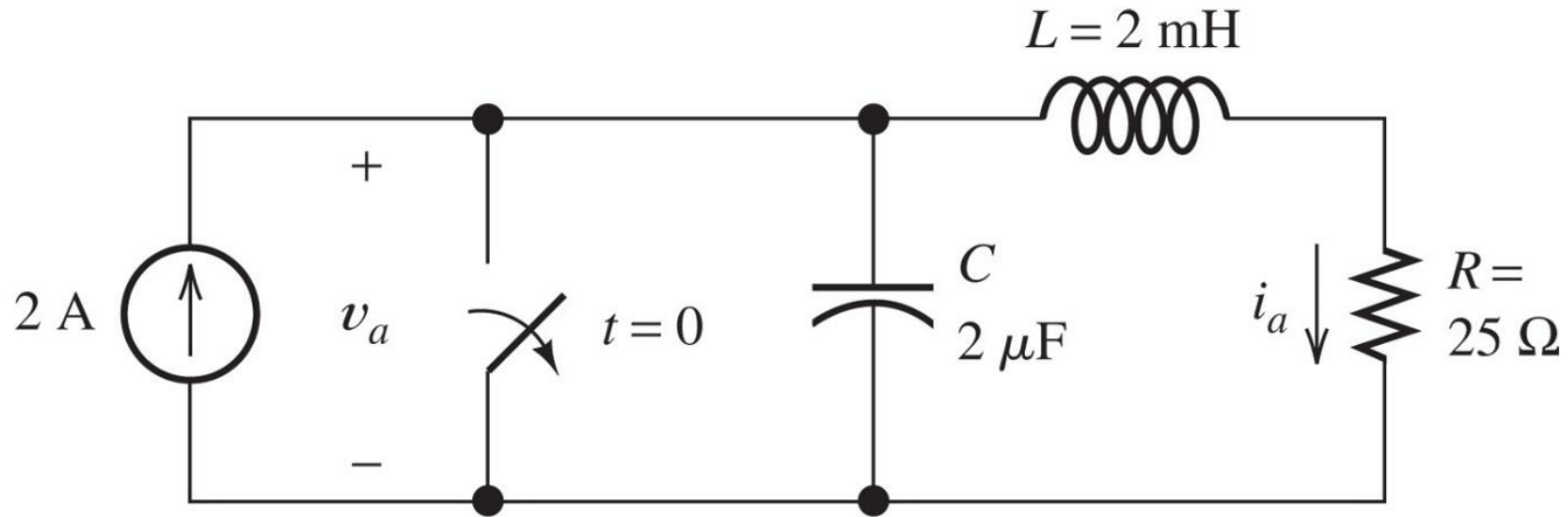EXERCISE (1)


Find the DC Steady-state values of v_a and i_a :



(a)

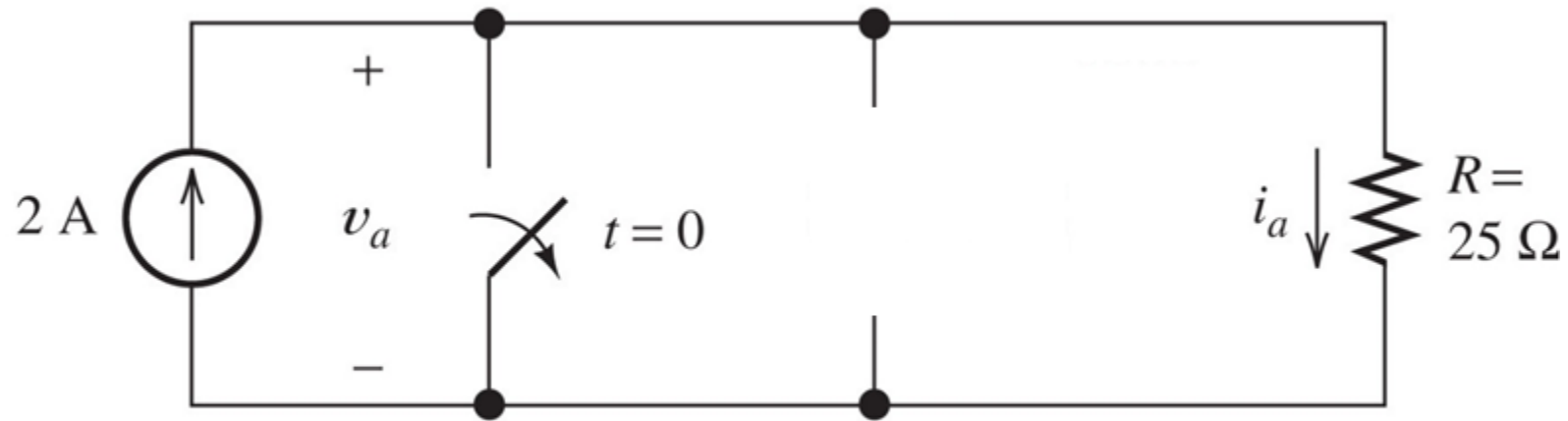EXERCISE (1) SOLVED


Find the DC Steady-state values of v_a and i_a :



(a)

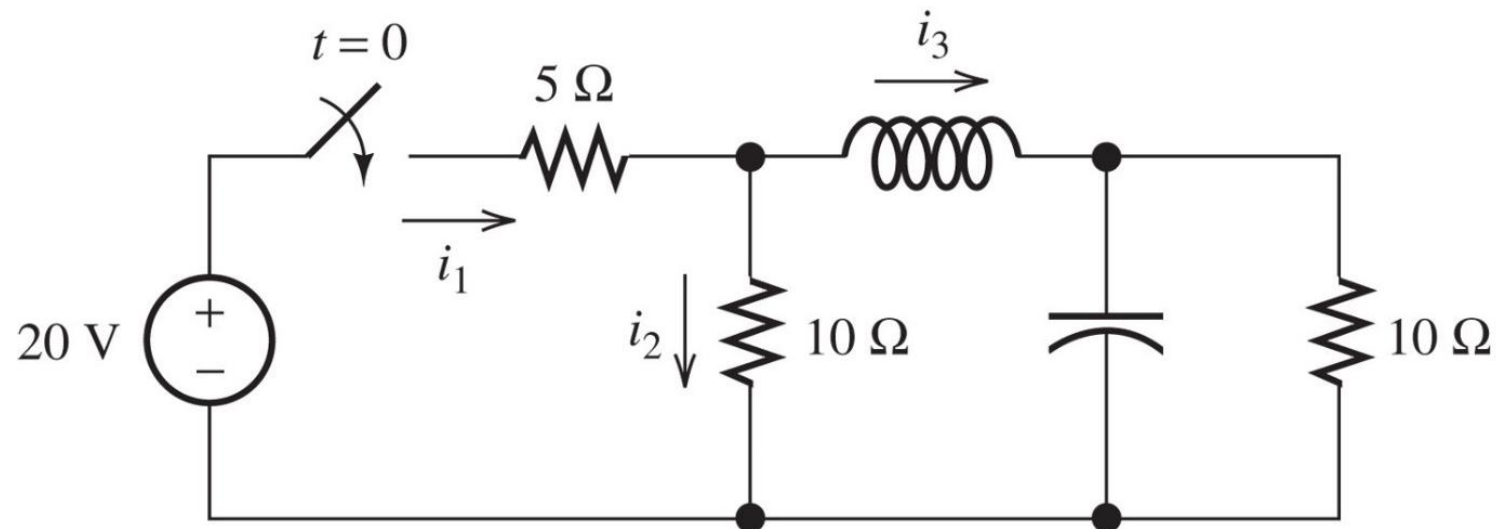EXERCISE (2)


Find the DC Steady-state values of i_1 and i_2 :



(b)

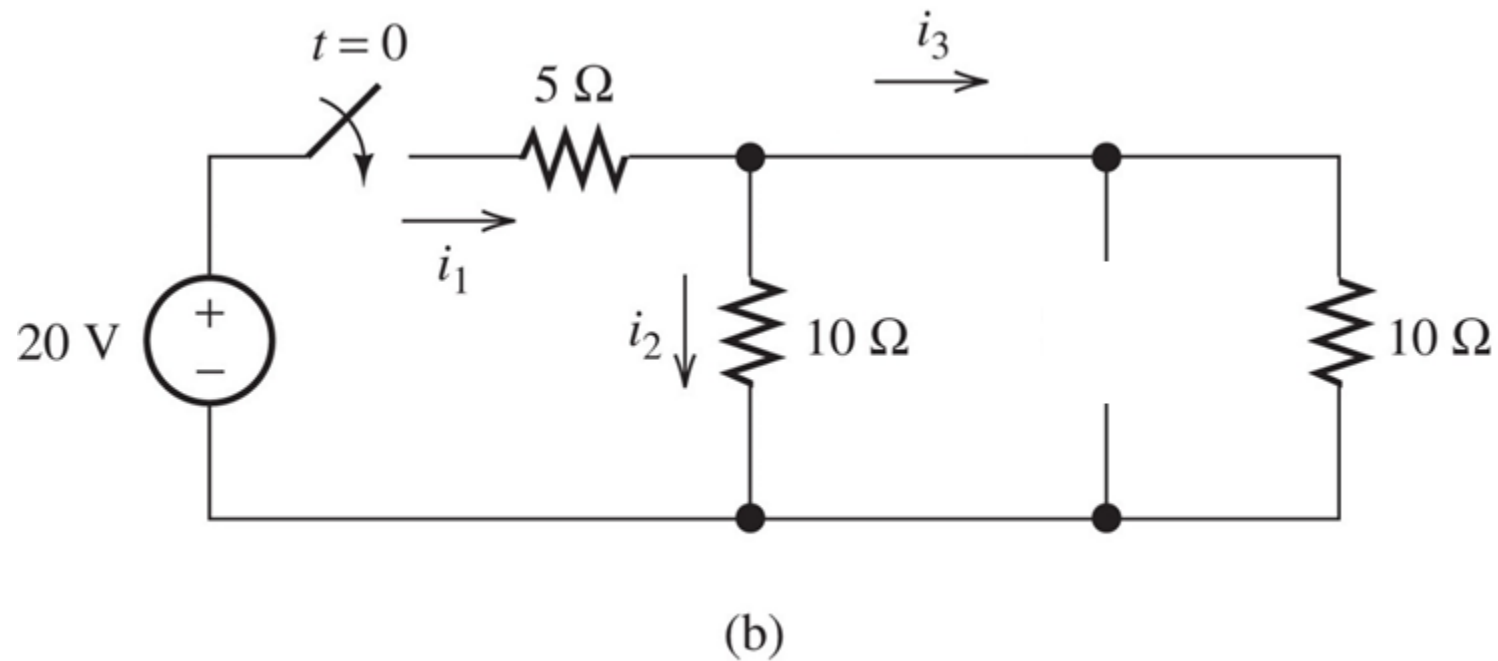EXERCISE (2) SOLVED

Find the DC Steady-state values of i_1 and i_2 :



PROBLEMS FOR THIS WEEK

- P4.22
- P4.23
- P4.25
- P4.28
- P4.30