

SCHOOL OF ENGINEERING, ELECTRICAL AND ELECTRONIC ENGINEERING

# NETWORKS 4\_

## Week E\_



Ronald van Buuren  
May 2023

## NET4 PROGRAM BY WEEK

1. 1<sup>st</sup> order RC networks – discharging – DC source
2. 1<sup>st</sup> order RC networks – charging –DC source
3. RL networks – Steady-state DC
4. RL networks – Switched DC source
5. RC & RL networks – complementary solution
6. <spare week>
7. Exam Prep

# CAPACITOR & INDUCTOR RELATIONS


	Capacitor	Inductor
Voltage	$v = \frac{1}{C} \int i(t) dt$	$v = L \frac{di}{dt}$
Current	$i = C \frac{dv}{dt}$	$i = \frac{1}{L} \int v(t) dt$
Power	$P(t) = v(t) \cdot i(t)$	
Energy	$W(t) = \frac{1}{2} C v^2(t)$	$W(t) = \frac{1}{2} L i^2(t)$
Energy stored in:	Electric field	Magnetic field

# WEEK D: SWITCHED DC SOURCE, RL CIRCUITS

At  $t = 0$  we close the switch

Inductor


$$v = L \frac{di}{dt}$$

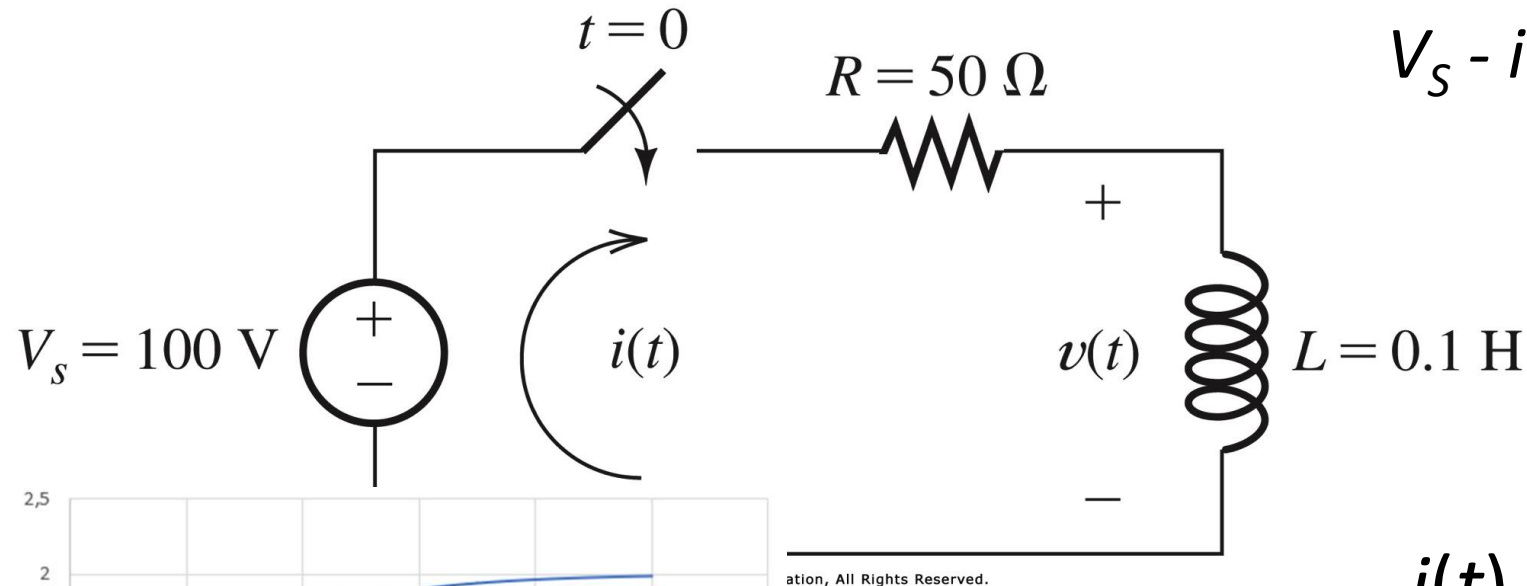

$$V_S - i(t) \cdot R - L \frac{di}{dt} = 0$$

$$i(t) + \frac{L}{R} \frac{di(t)}{dt} = \frac{V_S}{R}$$

$$i(t) = 2 - 2e^{-500t} \text{ A}$$

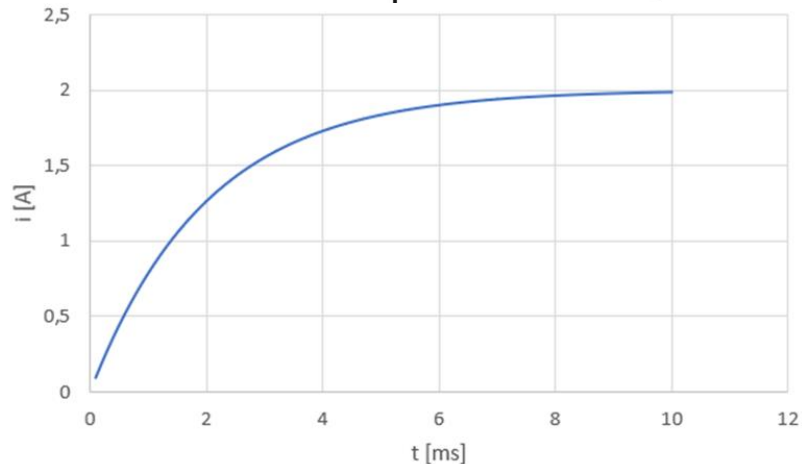


# THIS WEEK

- Find expressions for  $i(t)$  and  $v(t)$  using *just steady-state values*
  - *and smart reasoning* 😊
- Switching on AC sources

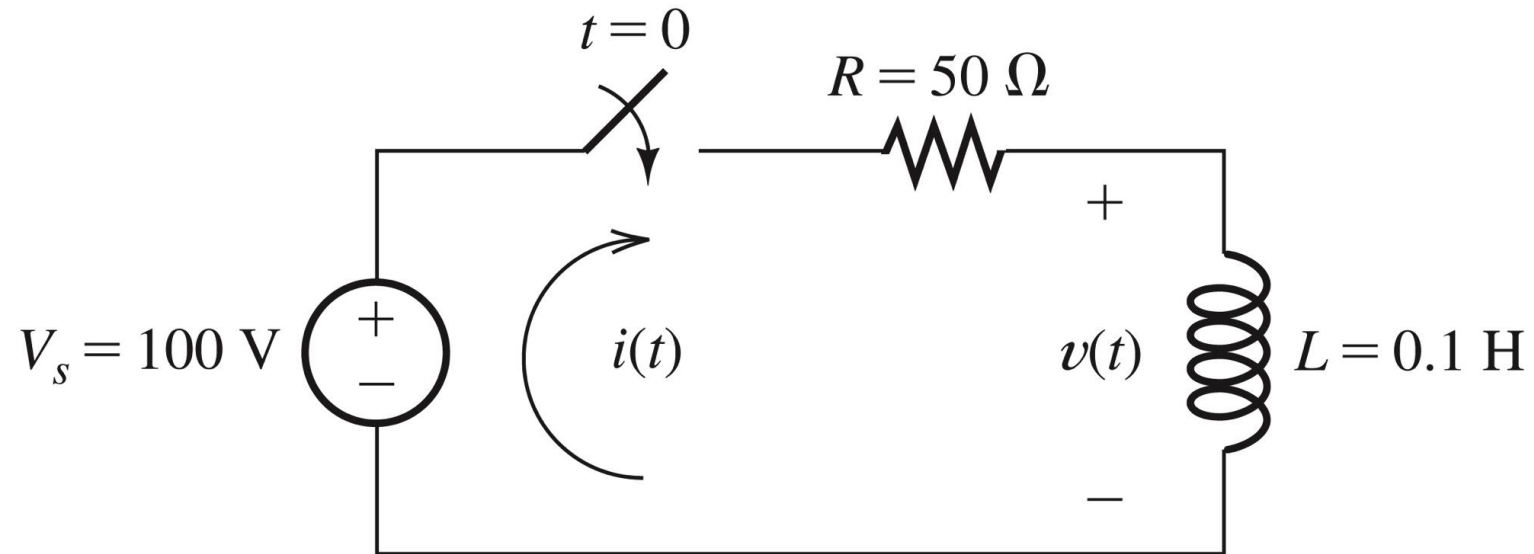
## RL CIRCUITS – VIA DC STEADY STATE

Find expressions for  $i(t)$  and  $v(t)$  for  $t > 0$



Copyright ©2018 Pearson Education, All Rights Reserved.

## RL CIRCUITS – VIA DC STEADY STATE

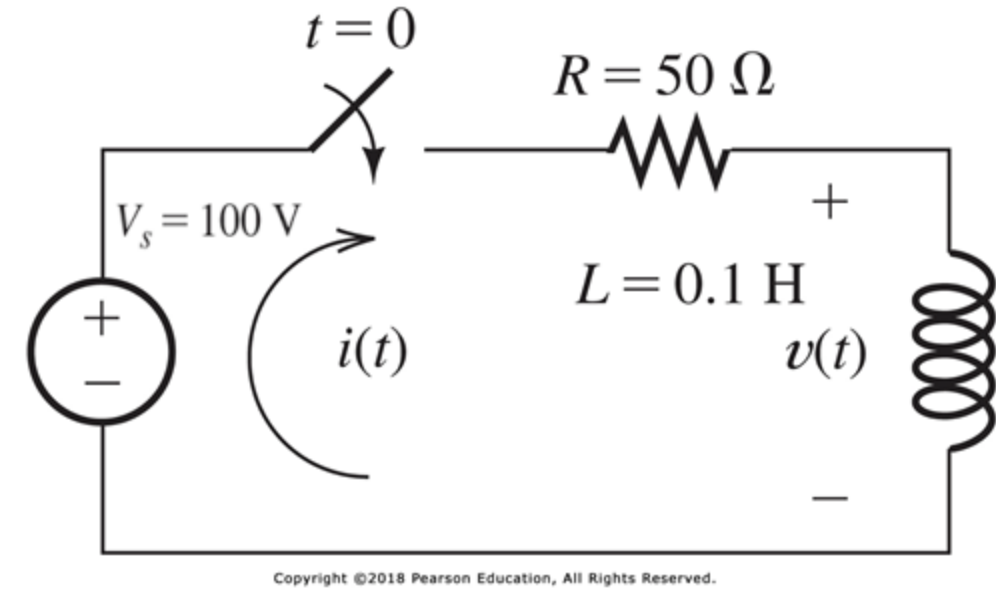

- at  $t = 0^-$  s,  $i(t) = 0$  A
- at  $t = \infty$ ,  $i(t) = 100/50 = 2$  A
- time constant  $\tau = L/R = 0.002$  s = 2 ms
- general form  $i(t) = K_1 + K_2 e^{-t/\tau}$
- we know all we need to know:
  - for  $t = \infty$ , we get  $K_1 = 2$  A
  - for  $t = 0^-$  s:  $K_1 + K_2 = 0 \rightarrow K_2 = -2$  A
- $i(t) = 2 - 2e^{-t/0.002} = 2 - 2e^{-500t}$

# GENERAL (AC) SOURCES

$$i(t) + \frac{L}{R} \frac{di(t)}{dt} = \frac{V_S}{R}$$

$$RC \frac{dv_C(t)}{dt} + v_C(t) = V_S$$

General form:

$$\tau \frac{dx(t)}{dt} + x(t) = f(t)$$

$\tau$	depends only on component values ( $\tau = RC$ , $\tau = L/R$ )
$x(t)$	$i(t)$ , $v(t)$ from circuit equations (KVL, KCL)
$f(t)$	source(s)



# COMPLEMENTARY SOLUTION

$$\tau \frac{dx(t)}{dt} + x(t) = f(t)$$

# COMPLEMENTARY SOLUTION

$$\tau \frac{dx(t)}{dt} + x(t) = 0$$

- Set the sources to 0: *homogeneous equation*
- Complementary Solution  $x_c(t) = Ke^{-\frac{t}{\tau}}$
- To be done: find  $K$ 
  - *from initial conditions (typically, at  $t = 0$  s)*

# PARTICULAR SOLUTION

Original (full) equation  $\tau \frac{dx(t)}{dt} + x(t) = f(t)$

- Do an intelligent guess that fits:  $x_p(t)$
- Be inspired by  $f(t)$  and its time derivatives
  - $f(t) = \textit{constant}$   $\rightarrow x_p(t) = A$
  - $f(t) = \textit{linear}$   $\rightarrow x_p(t) = A \cdot t + B$
  - $f(t) = \textit{quadratic}$   $\rightarrow x_p(t) = A \cdot t^2 + B \cdot t + C$
  - $f(t) = \textit{sinusoidal}$   $\rightarrow x_p(t) = A \sin \omega t + B \cos \omega t$

# COMBINE COMPLEMENTARY & PARTICULAR SOLUTIONS


Original (full) equation  $\tau \frac{dx(t)}{dt} + x(t) = f(t)$

- Sum complementary & particular solutions:
  - $x(t) = x_c(t) + x_p(t)$
- Now remember:  $x_c(t) = Ke^{-\frac{t}{\tau}}$ 
  - Need to find  $K$
  - *Use initial conditions*

## NEW RECIPE FOR SIMPLE CIRCUITS (RC & RL)

1. Use one of Kirchhoff's laws to get a circuit equation
2. If the equation has integrals, differentiate all terms to get a pure differential equation
  1. This will get you  $\tau$
3. Set the equation equal to 0 (homogeneous equation)
  1. *This will get you the Complementary Solution  $Ke^{-t/\tau}$*
4. Do an intelligent guess to solve the full equation
  1. *This will get you the Particular Solution*
5. Write the now fully known solution – Complementary + Particular
  1. using  $R, L, C, \tau, \dots$
6. Use starting conditions ( $t=0^-$ ,  $t=0^+$ ) to get  $K$

## EXAMPLE 4.6

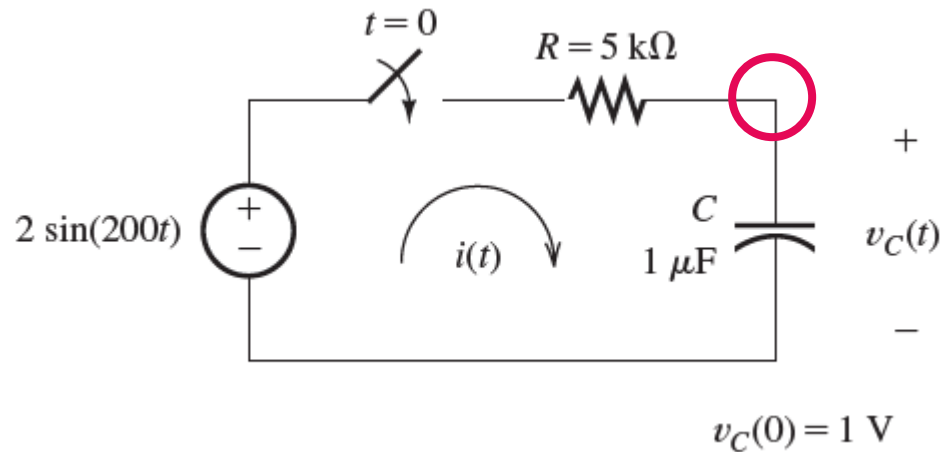

### Flashback from NET4 week B

1. KCL at top-right node: sum = 0
  1. incoming:  $(v_C(t) - V_s)/R$
  2. outgoing:  $C \cdot dv_C/dt$


$$C \frac{dv_C(t)}{dt} + \frac{v_C(t) - V_s}{R} = 0$$

Capacitor
$v = \frac{1}{C} \int i(t) dt$
$i = C \frac{dv}{dt}$
$P(t) =$

$$RC \frac{dv_C(t)}{dt} + v_C(t) = 2 \sin(200t)$$

3. Set the equation equal to 0 (homogeneous equation)
  1. This will get you the Complementary Solution  $Ke^{-t/\tau}$
4. Do an intelligent guess to solve the full equation
  1. This will get you the Particular Solution
5. Write the now fully known solution – Complementary + Particular
  1. using  $R, L, C, \tau, \dots$
6. Use starting conditions ( $t=0^-$ ,  $t=0^+$ ) to get  $K$

## EXAMPLE 4.6

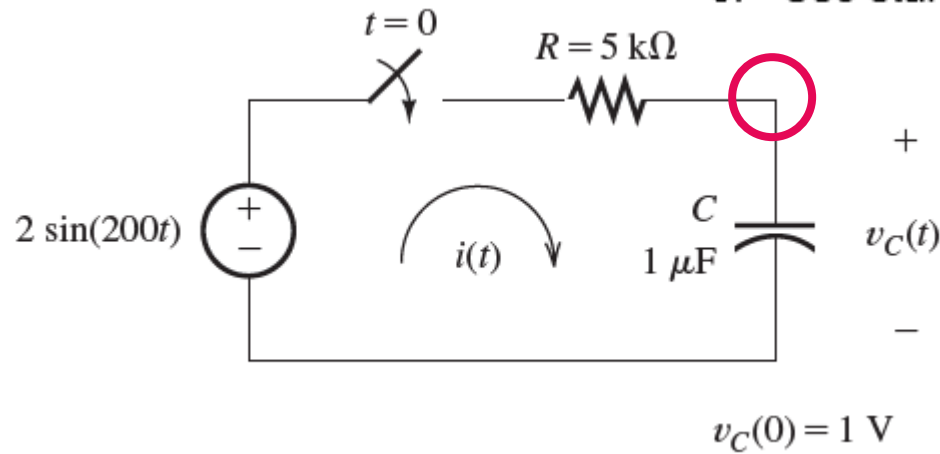

Apply the recipe step 3


$$RC \frac{dv_C(t)}{dt} + v_C(t) = 0$$

Compl. Sol.  $v_{CC}(t) = Ke^{-t/RC}$

$$RC \frac{dv_C(t)}{dt} + v_C(t) = 2 \sin(200t)$$

3. Set the equation equal to 0 (homogeneous equation)
  1. This will get you the Complementary Solution  $Ke^{-t/\tau}$
4. Do an intelligent guess to solve the full equation
  1. This will get you the Particular Solution
5. Write the now fully known solution – Complementary + Particular
  1. using  $R, L, C, \tau, \dots$
6. Use starting conditions ( $t=0^-$ ,  $t=0^+$ ) to get  $K$

## EXAMPLE 4.6

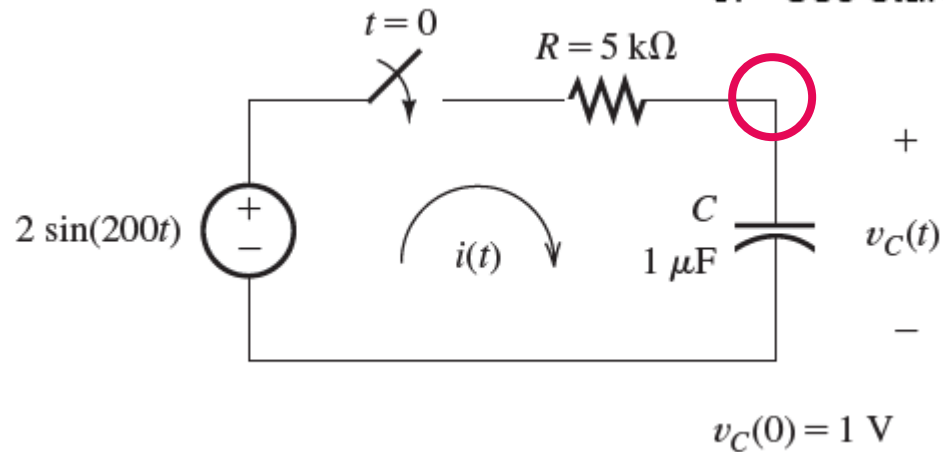

**Apply the recipe step 4**

$$RC \frac{dv_C(t)}{dt} + v_C(t) = 2 \sin(200t)$$

*Partic. Sol.*  $v_{CP}(t) = A \sin 200t + B \cos 200t$

1. substitute into equation
2. turns out:  $A = 1$   $B = -1$


So:  $v_{CP}(t) = \sin 200t - \cos 200t$

$$RC \frac{dv_C(t)}{dt} + v_C(t) = 2 \sin(200t)$$



3. Set the equation equal to 0 (homogeneous equation)
  1. This will get you the Complementary Solution  $Ke^{-t/\tau}$
4. Do an intelligent guess to solve the full equation
  1. This will get you the Particular Solution
5. Write the now fully known solution – Complementary + Particular
  1. using  $R, L, C, \tau, \dots$
6. Use starting conditions ( $t=0^-$ ,  $t=0^+$ ) to get  $K$

## EXAMPLE 4.6

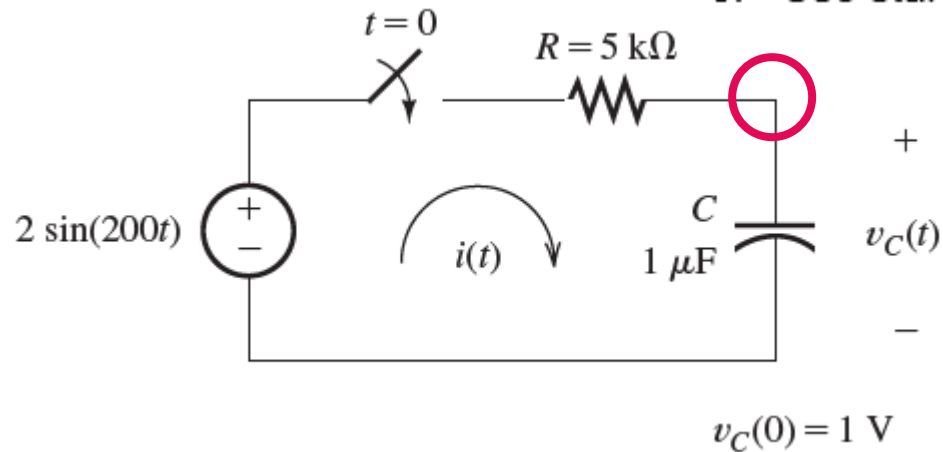

**Apply the recipe step 5**

*Compl. Sol.*  $v_{CC}(t) = Ke^{-t/RC}$


*Partic. Sol.*  $v_{CP}(t) = \sin 200t - \cos 200t$

$v_C(t) = Ke^{-t/RC} + \sin 200t - \cos 200t$

$$RC \frac{dv_C(t)}{dt} + v_C(t) = 2 \sin(200t)$$

3. Set the equation equal to 0 (homogeneous equation)
  1. This will get you the Complementary Solution  $Ke^{-t/\tau}$
4. Do an intelligent guess to solve the full equation
  1. This will get you the Particular Solution
5. Write the now fully known solution – Complementary + Particular
  1. using  $R, L, C, \tau, \dots$
6. Use starting conditions ( $t=0^-$ ,  $t=0^+$ ) to get  $K$

## EXAMPLE 4.6

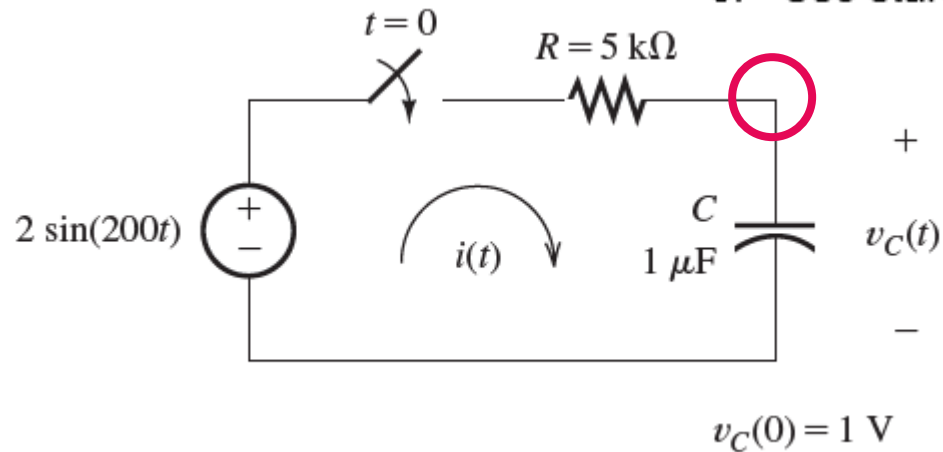

**Apply the recipe step 6**

$$v_C(t) = Ke^{-t/RC} + \sin 200t - \cos 200t$$

At  $t = 0 \text{ s}$ ,  $v_C(t) = 1 \text{ V}$


- $K + 0 - 1 = 1$
- $\rightarrow K = 2$

$$\begin{aligned} v_C(t) &= 2e^{-t/RC} + \sin 200t - \cos 200t \\ &= 2e^{-200t} + \sin 200t - \cos 200t \end{aligned}$$

$$RC \frac{dv_C(t)}{dt} + v_C(t) = 2 \sin(200t)$$

3. Set the equation equal to 0 (homogeneous equation)
  1. This will get you the Complementary Solution  $Ke^{-t/\tau}$
4. Do an intelligent guess to solve the full equation
  1. This will get you the Particular Solution
5. Write the now fully known solution – Complementary + Particular
  1. using  $R, L, C, \tau, \dots$
6. Use starting conditions ( $t=0^-$ ,  $t=0^+$ ) to get  $K$

## EXAMPLE 4.6

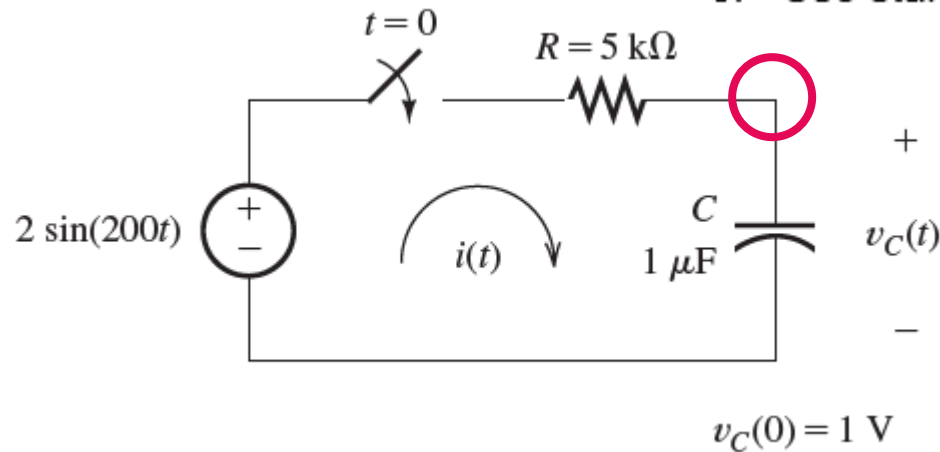

**Check Hambley's answer for  $i(t)$**

$$v_C(t) = 2e^{-200t} + \sin 200t - \cos 200t$$

$$\begin{aligned} i(t) &= C \cdot dv_C(t)/dt \\ &= C \cdot [-400e^{-200t} + 200\cos 200t + 200\sin 200t] \text{ A} \\ &= -400e^{-200t} + 200\cos 200t + 200\sin 200t \text{ } \mu\text{A} \end{aligned}$$

$$i(t) = 200 \cos(200t) + 200 \sin(200t) - 400e^{-t/RC} \text{ } \mu\text{A} \quad (4.56)$$

$$RC \frac{dv_C(t)}{dt} + v_C(t) = 2 \sin(200t)$$

# PROBLEMS FOR THE EXERCISES SESSION

- P4.45
- P4.47
- P4.49
- P4.50
- P4.51
- P4.54