

SCHOOL OF ENGINEERING, ELECTRICAL AND ELECTRONIC ENGINEERING

NETWORKS 4_

Week B_



Ronald van Buuren
April 2023


NET4 PROGRAM BY WEEK

1. 1st order RC networks – discharging – DC source
2. 1st order RC networks – charging – DC source
3. RL networks – Steady-state DC
4. RL networks – Switched DC source
5. RC & RL networks – complementary solution
6. <spare week>
7. Exam Wrapup

WEEK A: CAPACITOR & INDUCTOR


	Capacitor	Inductor
Voltage	$v = \frac{1}{C} \int i(t) dt$	$v = L \frac{di}{dt}$
Current	$i = C \frac{dv}{dt}$	$i = \frac{1}{L} \int v(t) dt$
Power	$P(t) = v(t) \cdot i(t)$	
Energy	$W(t) = \frac{1}{2} C v^2(t)$	$W(t) = \frac{1}{2} L i^2(t)$
Energy stored in:	Electric field	Magnetic field

WEEK A: DISCHARGING A CAPACITOR

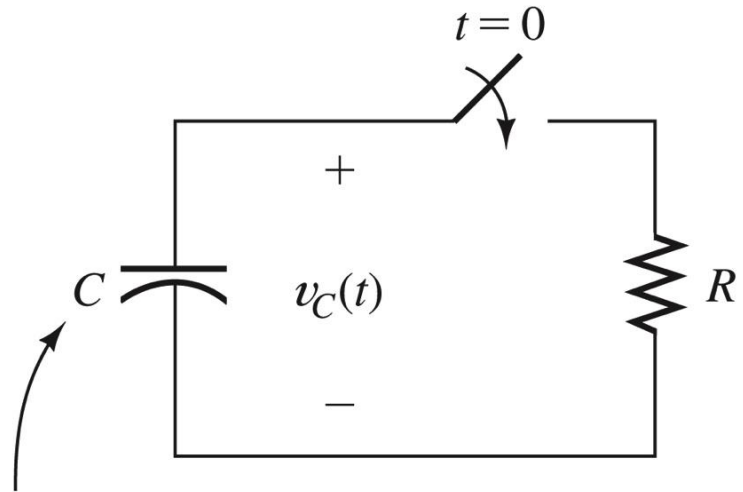

Capacitance charged to V_i
prior to $t = 0$

$$RC \frac{dv_C(t)}{dt} + v_C(t) = 0$$

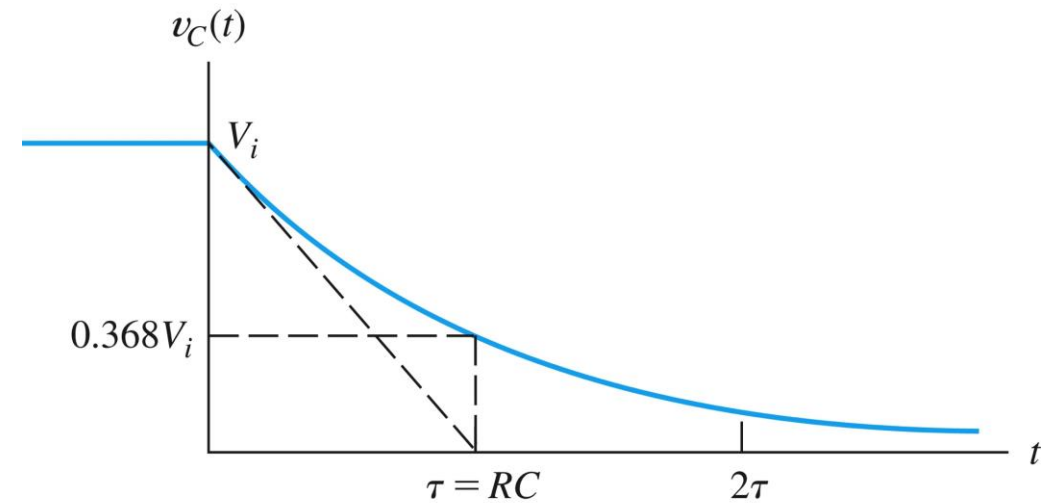

Copyright ©2018 Pearson Education, All Rights Reserved.

$$v_C(t) = V_i e^{-t/RC}$$


$$\tau = RC$$

THIS WEEK

1st order networks with a fixed DC source


- Charging a capacitor

CHARGING A CAPACITOR

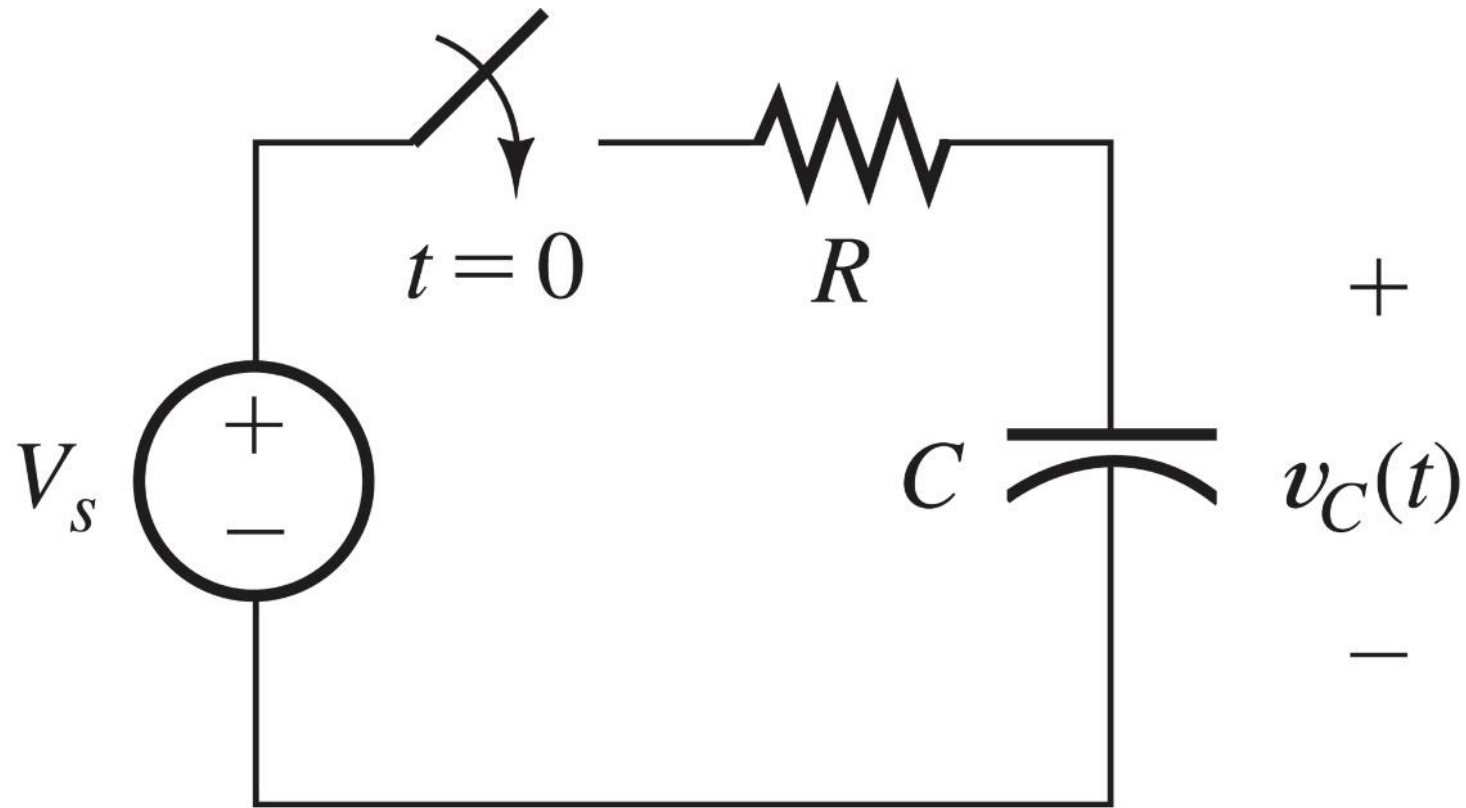

Copyright ©2018 Pearson Education, All Rights Reserved.

CHARGING A CAPACITOR: KCL

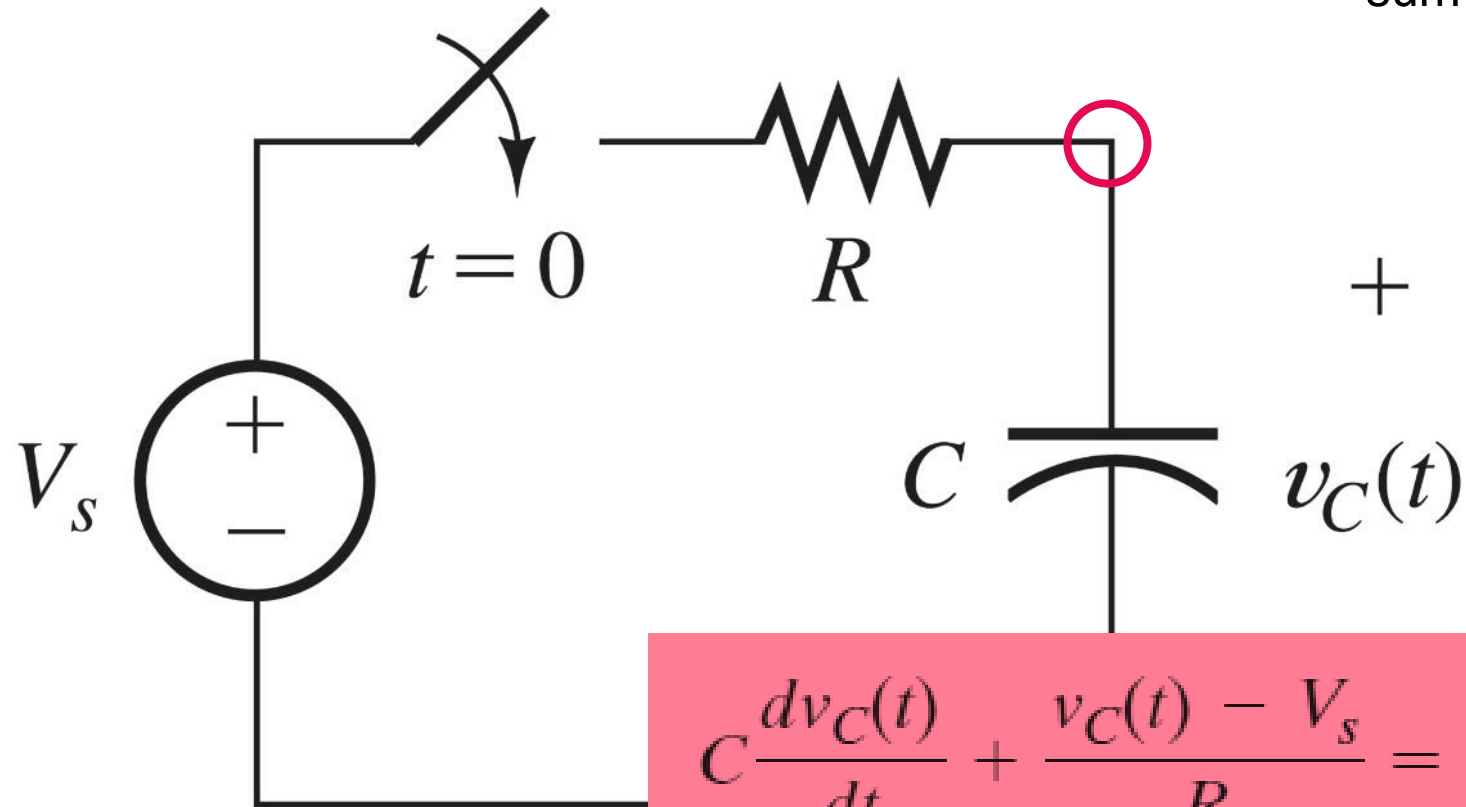

KCL:

- sum of currents = 0

Capacitor
$v = \frac{1}{C} \int i(t) dt$
$i = C \frac{dv}{dt}$
$P(t) =$

$$C \frac{dv_C(t)}{dt} + \frac{v_C(t) - V_s}{R} = 0$$

(4.10)

CHARGING A CAPACITOR: KCL


$$C \frac{dv_C(t)}{dt} + \frac{v_C(t) - V_s}{R} = 0 \quad (4.10)$$

$$RC \frac{dv_C(t)}{dt} + v_C(t) = V_s \quad (4.11)$$


Educated guess $v_C = K_1 + K_2 e^{st}$

$$v_C(t) = V_s - V_s e^{-t/RC} \quad (4.19)$$

CHARGING A CAPACITOR

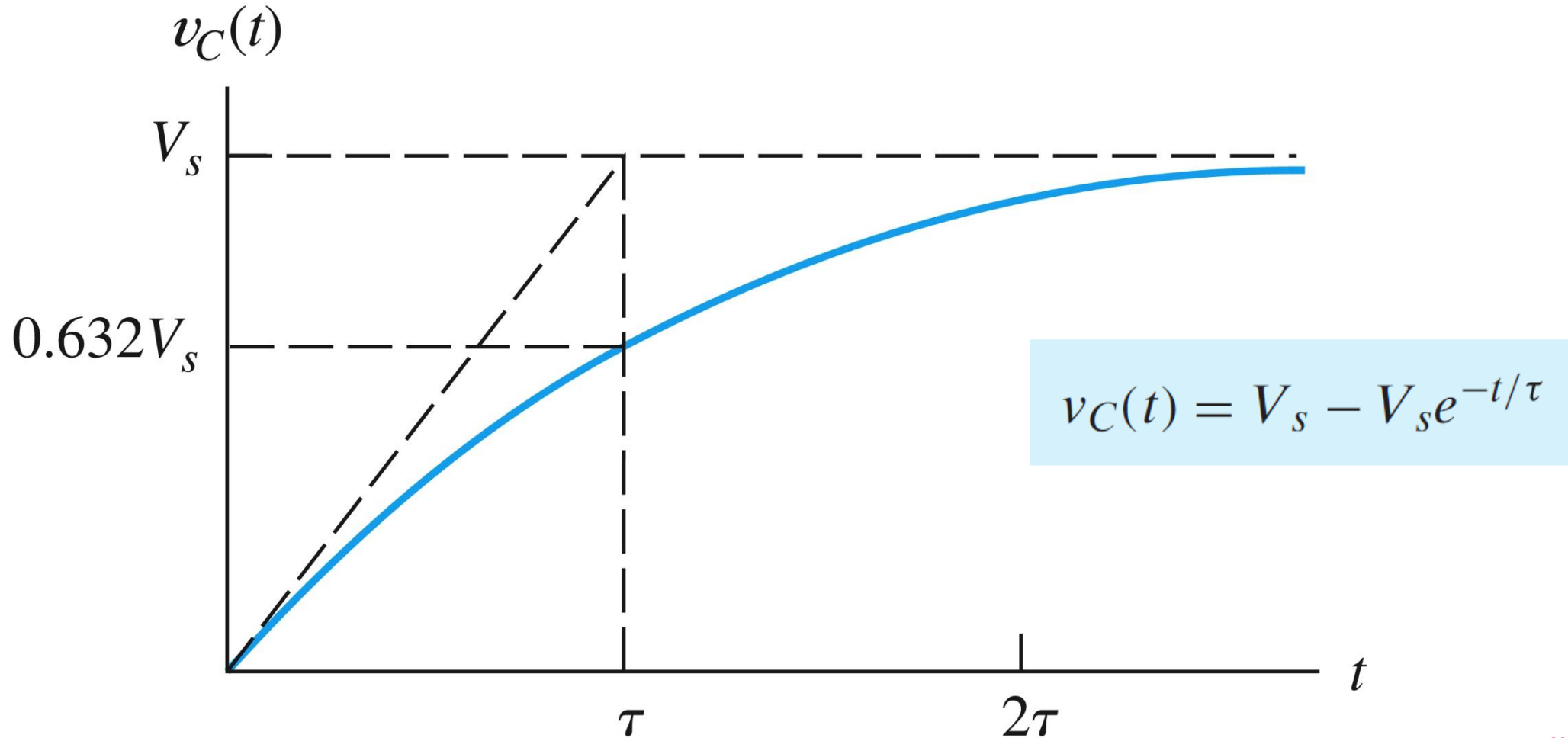

EXAMPLE 4.2

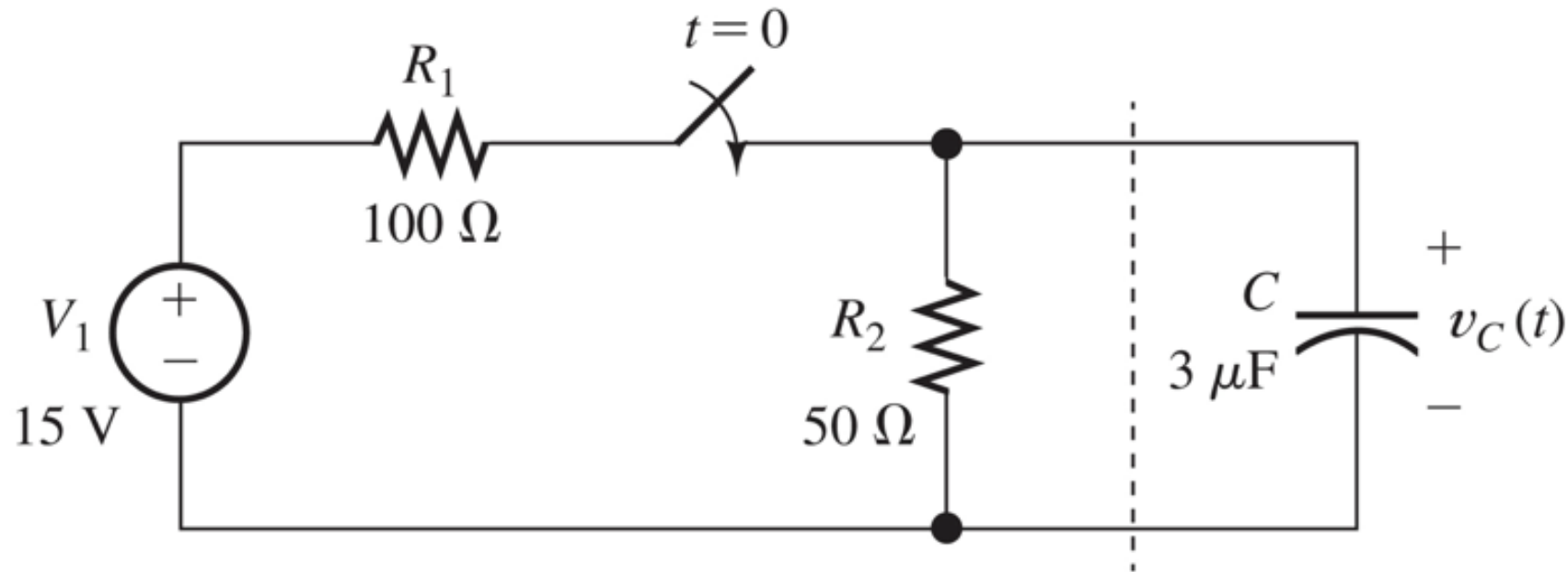


Example 4.2 First-Order RC Circuit

The switch in the circuit of Figure 4.5(a) has been open for a very long time prior to $t = 0$ and closes at $t = 0$. Find an expression for $v_C(t)$ for $t > 0$.

EXAMPLE 4.2 SOLUTION

- Thévenin equivalent

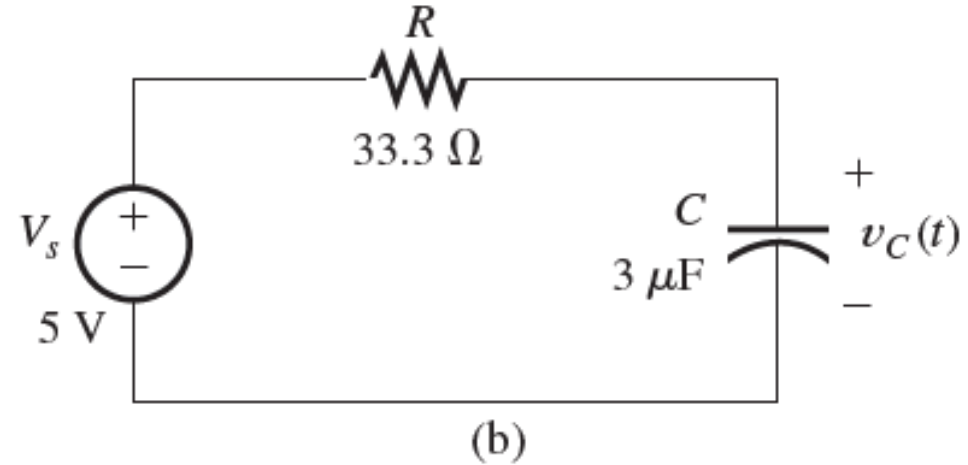


- KCL – or rather, realize that this is a standard 1st order RC circuit in CHARGING mode

$$v_C(t) = V_s - V_s e^{-t/\tau}$$

EXERCISE

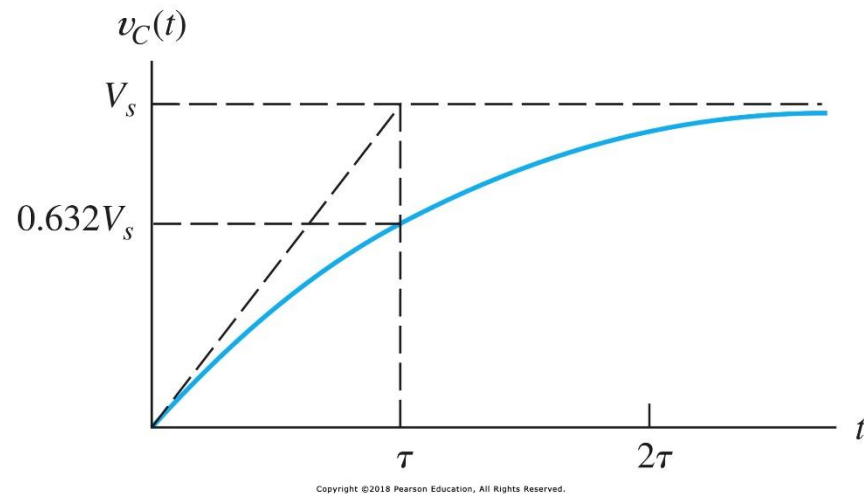
Exercise 4.2 Show that if the initial slope of $v_C(t)$ is extended, it intersects the final value at one time constant, as shown in Figure 4.4. [The expression for $v_C(t)$ is given in Equation 4.20.] □



$$v_C(t) = V_s - V_s e^{-t/\tau}$$

EXERCISE 4.2 – SOLUTION STEP 1

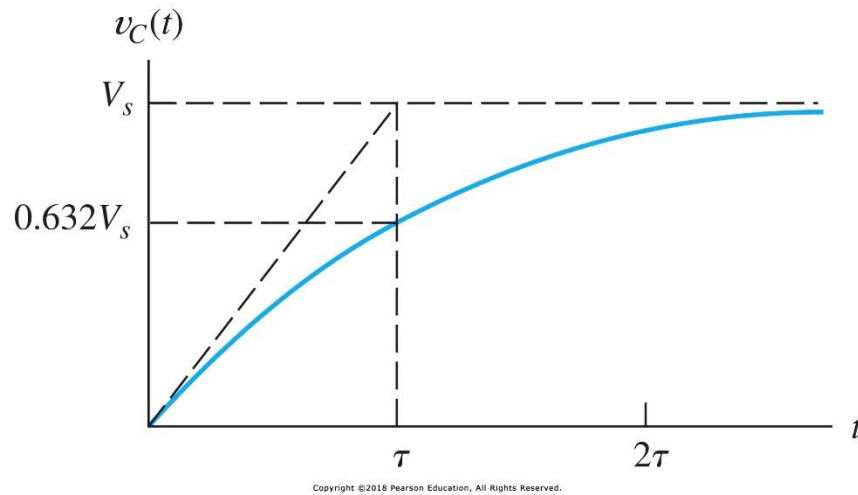Exercise 4.2 Show that if the initial slope of $v_C(t)$ is extended, it intersects the final value at one time constant, as shown in Figure 4.4. [The expression for $v_C(t)$ is given in Equation 4.20.] □



$$v_C(t) = V_s - V_s e^{-t/\tau}$$

$$v_C(t) = V_s(1 - e^{-t/\tau})$$

$$\text{slope: } \frac{dv_C}{dt} = V_s \frac{d(1 - e^{-t/\tau})}{dt} = V_s \frac{1}{\tau} e^{-t/\tau}$$

$$\text{so, at } t=0: \text{slope} = \frac{V_s}{\tau}$$

PROBLEMS

- P4.3
- P4.8
- P4.13
- P4.14
- P4.17
- P4.18